

**LINEAR AND DIGITAL INTEGRATED CIRCUITS**

## Instructions:-

1. Last date of Submission **22<sup>nd</sup> March 2020 (SUNDAY)**.
2. All problems are compulsory.
3. Write your name and class roll number on the top of every page containing solution.
4. Only soft copy in a single PDF format is to be uploaded on whatsapp group.

Maximum Marks:- 10

Q1. Number system and codes:-

2M

- (a)  $9F2_{16} = ?_2 = ?_{10}$
- (b)  $0110100000111001_2 = ?_{BCD}$
- (c) Solve using 2's complement method
  1. Add  $59_{10}$  and  $38_{10}$
  2. Subtract  $39_{10}$  from  $-59_{10}$

Q2. Solve the given expression using K-map and draw the equivalent NAND – NAND circuit diagram.  $Y(A,B,C,D) = \sum (1,5,6,7,11,12,13,15)$  2M

Q3. Construct a 4-bit binary adder subtractor and explain its working.

1M

Q4. Construct a MOD – 10 counter and explain its working

1M

Q5. Draw the circuit diagram and explain the working of a JK flip flop with asynchronous inputs to the flip flops? 2M

Q6. Draw the circuit for D/A convertor and explain its working.

2M