
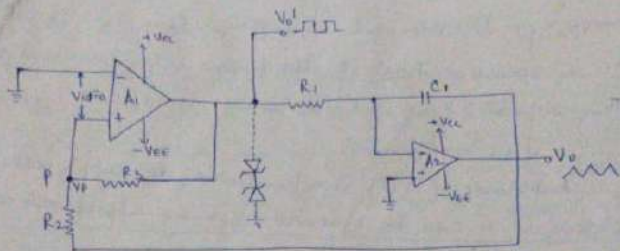


(6)

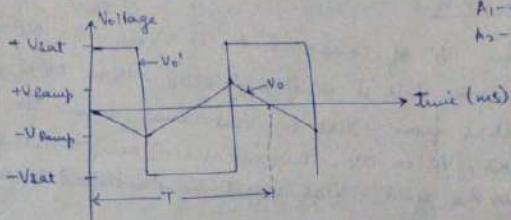


A₁ - comparator
A₂ - integrator



A₁ compares the voltage at P with the inverting SIP that is 0V. When V_P goes slightly below 0V, the O/P of A₁ is at the negative saturation & when V_P goes slightly above 0V, O/P of A₁ goes to +ve saturation level.

If A₁ is at +ve sat, +V_{sat} ($\cong +V_{CC}$); SIP to A₂ is +V_{sat}, \therefore the O/P of A₂ will be a negative going Ramp. Thus one end of voltage divider R₂-R₃ is the positive saturation voltage +V_{sat} of A₁ and the other is the negative going Ramp of A₂. When this Ramp attains a value of -V_{ramp}, point P is slightly below 0V. Hence O/P of A₁ switches from +ve saturation to -ve saturation -V_{sat} ($\cong -V_{EE}$). \therefore O/P of A₂ will now begin

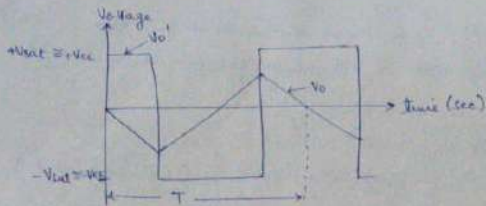

For o/p of A_2 to be triangular, $5R_2C_2 > T/2$

Generally $R_3C_2 = T$

For stable Δ o/p, shunt C_2 with $R_4 (= 10R_3)$
and connect an offset compensating N/O at the noninverting o/p of A_2 .

Freq. of Δ wave generator is limited by the slew rate of the op-amp (as in any oscillator). \therefore high slew rate op-amp like LM301 is used for generating higher freq.


Another Δ wave generator which uses lesser no. of components can also be used. It consists of a comparator and an integrator

Sawtooth Wave Generator

In Δ wave, rise time = fall time

Sawtooth wave has unequal rise & fall times.

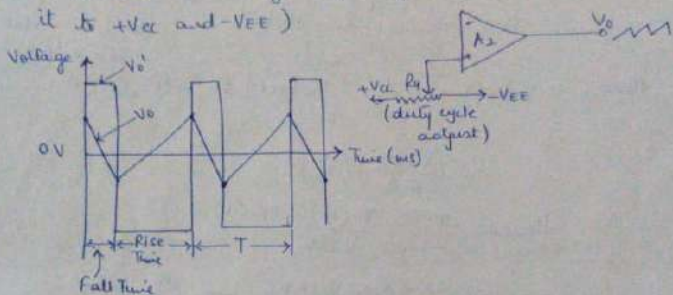The ckt. is same as ~~same~~ Δ wave generator except that the non-inverting terminal of A_2 is connected to a variable dc voltage (by using potentiometer & connecting it to $+V_{cc}$ and $-V_{EE}$).



Depending on the R_4 setting, a certain dc level is inserted in the o/p of A_2 . This would mean that o/p of A_2 will be a Δ wave riding on some dc level that is a function of the R_4 setting. The duty cycle of the square wave will be determined by the polarity and amplitude of this dc level. A duty cycle $< 50\%$ causes o/p of A_2 to be a sawtooth. Wiper of R_4 in the center gives o/p of A_2 as a Δ wave. When wiper of R_4 moves towards $-V_{EE}$, Rise time $>$ Fall Time. If wiper moves towards $+V_{cc}$, Fall time $>$ Rise Time

Amplitude of Sawtooth wave is independent of R_4 setting

to go positively. This continues till A_2 reaches $+V_{Ramp}$. At this pt. P is slightly above $0V$, \therefore o/p of A_1 is switched back to the positive saturation level $+V_{sat}$. This repeats & we get the above waveform.

$$f_{out} = f_{in}$$

Amplitude of JTL is a function of dc supply voltages; a desired " can be obtained by using appropriate values of the o/p of A_1 .

* When o/p of comparator A_1 is $+V_{sat}$, the o/p of A_2 decreases till it reaches $-V_{Ramp}$. Here o/p of A_1 switches from $+V_{sat}$ to $-V_{sat}$. Just before the switching occurs, V_p is $0V$. This means $-V_{Ramp}$ must be developed across R_2 and $+V_{sat}$ must be developed across R_3 .

$$\therefore \frac{-V_{Ramp}}{R_2} = -\frac{+V_{sat}}{R_3}$$

$$\text{or } -V_{Ramp} = -\frac{R_2}{R_3} (+V_{sat}) \quad \text{--- (1)}$$

Similarly, $+V_{Ramp}$, the o/p of A_2 at which o/p of A_1 switches from $-V_{sat}$ to $+V_{sat}$ is,

$$+V_{Ramp} = -\frac{R_2}{R_3} (-V_{sat}) \quad \text{--- (2)}$$

\therefore peak-to-peak o/p amplitude of Δ o/p is

$$V_o(p-p) = +V_{Ramp} - (-V_{Ramp})$$

$$\boxed{V_o(p-p) = 2 \frac{R_2}{R_3} (V_{sat})} \quad \text{--- (3)}$$

Q) Design the square wave osc. so that $f_0 = 1\text{KHz}$.
 op-amp used is 741 with dc supply voltages $= \pm 15\text{V}$.

Ans) Use $R_2 = 1.16 R_1$

let $R_1 = 10\text{K}\Omega$

Then, $R_2 = (1.16)(10) = 11.6\text{K}\Omega$ ($R_2 = 20\text{K}\Omega$ pot)


Next, choose $C = 0.05\ \mu\text{F}$, $f_0 = \frac{1}{2RC}$

$$R = \frac{1}{2f_0 C} = \frac{1}{2 \times 10^3 \times 0.05 \times 10^{-6}} = 10\text{K}\Omega$$

Thus $R_1 = 10\text{K}\Omega$, $R_2 = 11.6\text{K}\Omega$, $R = 10\text{K}\Omega$, $C = 0.05\ \mu\text{F}$.

Triangular Wave Generator

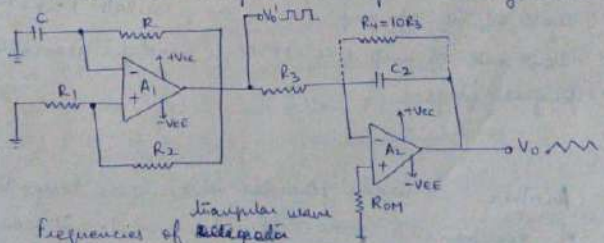① Connect an integrator to a square wave generator.



Triangular wave frequencies of ~~integrator~~

& square wave generator is the same. for fixed R_1, R_2, C the freq. of square & triangular wave depends on \underline{R}

$$f_0 = \frac{1}{2RC \ln\left(\frac{2R_1 + R_2}{R_2}\right)}$$

Although amplitude of square wave is constant ($\pm V_{sat}$), the amp. of Δ wave decreases with \uparrow in freq. & viceversa

the o/p of the op-amp is forced to switch to a negative saturation, $-V_{sat}$. When V_o is at $-V_{sat}$, V_1 across R_1 is also negative, since

$$V_1 = \frac{R_1}{R_1 + R_2} (-V_{sat})$$

Thus $V_{id} = V_1 - V_2$ is negative which holds the V_o at $-V_{sat}$. O/P remains at $-V_{sat}$ till capacitor C discharges and then recharges to a -ive voltage slightly higher than $-V_1$.

As soon as capacitor's voltage V_2 becomes more negative than $-V_1$, V_{id} becomes positive.

$$\left\{ V_{id} = [V_1] - [V_2] = V_1 - (-V_2) = V_1 + V_2 = +ive. \right\}$$

and hence drives the o/p of the op-amp back to its +ive saturation $+V_{sat}$. This completes one cycle.

With o/p at $+V_{sat}$; V_1 (at noninverting o/p) = $\frac{R_1}{R_1 + R_2} (+V_{sat})$

Time period of the o/p waveform is,

$$T = 2RC \ln \left(\frac{2R_1 + R_2}{R_2} \right)$$

$$\text{or } f_0 = \frac{1}{2RC \ln \left[(2R_1 + R_2) / R_2 \right]}$$

$\Rightarrow f_0 = f_{max} [RC \text{ time constant, } R_1 \& R_2]$.



if, $R_2 = 1.16 R_1$,

$$\text{Then } f_0 = \frac{1}{2RC}$$

Smaller the time constant RC , higher is the o/p freq. f_0 .

If o/p is operated at higher freq., o/p becomes Triangular.

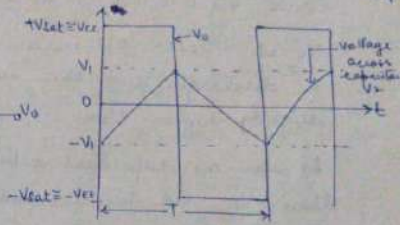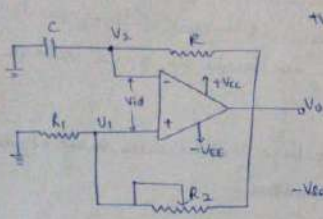Square Wave Generator :- Square wave o/p are generated when the op-amp is forced to operate in the saturated region. o/p is forced to swing repeatedly between +ve saturation $+V_{sat} (\approx V_{CC})$ and $-V_{sat} (\approx -V_{EE})$. It is also called a free running or astable Multivibrator. o/p is $+V_{sat}$ or $-V_{sat}$ depending on whether V_{id} is +ve or -ve.



$$|V_i| = \frac{R_1}{R_1 + R_2} |V_{sat}|$$

$$f_0 = \frac{1}{T} = \frac{1}{2RC} \text{ if } R_2 = 1.6R_1$$

Assume that voltage across cap. = 0V at the instant the dc supply voltages $+V_{CC}$ & $-V_{EE}$ are applied \Rightarrow Voltage at the Inverting O/P terminal = 0 initially.

At the same time, V_i at the noninverting terminal is a very small finite value which is a function of O/P offset voltage V_{OOT} and values of R_1 and R_2 . Thus $V_{id} = V_i$ at noninverting terminal. Thus V_i starts to drive the op-amp into saturation. e.g. if V_{OOT} is positive, V_i is also +ve. Initially C acts as a short ckt, gain of the op-amp (A) is very large; hence V_i drives o/p to $+V_{sat}$. With the o/p voltage of the op-amp at $+V_{sat}$, C starts charging towards $+V_{sat}$ through R . As soon as V_2 across C is slightly more positive than V_i ,

(9)

where $V_{sat} = |+V_{sat}| = |-V_{sat}|$

so amplitude of Δ wave decreases with an increase in R_3 .

Time it takes for the OP waveform to swing from $-V_{ramp}$ to $+V_{ramp} = 1/2$ the time period $T/2$.

We know that the integrator OP is,

$$V_o = \frac{-1}{RC} \int_0^t V_{in} \cdot dt + C$$

Here $V_i = -V_{sat}$
 $V_o = V_o(P-P)$

Here, $V_o(P-P) = \frac{-1}{R_1 C_1} \int_0^{T/2} (-V_{sat}) dt$ — (4) $\because C = 0$

$$= \left(\frac{V_{sat}}{R_1 C_1} \right) \left(\frac{T}{2} \right)$$

Hence $\frac{T}{2} = \frac{V_o(P-P) (R_1 C_1)}{V_{sat}}$

$$T = 2 R_1 C_1 \frac{V_o(P-P)}{V_{sat}} \quad \text{--- (5)}$$

where $V_{sat} = |+V_{sat}| = |-V_{sat}|$

substitute the value of $V_o(P-P)$ in (5) from (4),

$$T = \frac{2 R_1 C_1}{V_{sat}} \left(\frac{2 R_3 V_{sat}}{R_3} \right)$$

$$T = \frac{4 R_1 C_1 R_3}{R_3} \quad \text{--- (6)}$$

Freq. of oscillation, $f_o = \frac{R_3}{4 R_1 C_1 R_2}$

$f_o \uparrow$ with \uparrow in R_3

(6)



Aslāble Applications :-

① Square wave Dsc:

② free Running Ramp Generati

Astable Multivibrator \rightarrow free running operation (3)

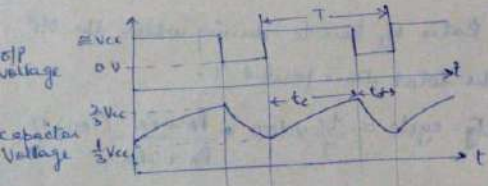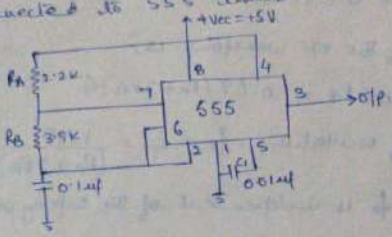- \rightarrow rectangular wave generating ckt.
- \rightarrow does not require external trigger to change the state of the OP.
- \rightarrow Time during which the OP is H or L is determined by 2 resistors and a capacitor, which are externally connected to 555 timer.



Initially, when OP is H, C starts charging towards V_{cc} through R_A and R_B .

As voltage across C, $V_c = \frac{2}{3} V_{cc}$, comparator 1 triggers the FF, and OP switches low. Now C starts discharging through R_B and Q_1 . When the $V_c = \frac{1}{3} V_{cc}$, comparator 2's OP triggers the FF, & OP goes HIGH. Then the cycle repeats.

C is repeatedly charged & discharged between $\frac{2}{3} V_{cc}$ and $\frac{1}{3} V_{cc}$ resp.

Time during which C charges, $\frac{1}{3}V_{cc}$ to $\frac{2}{3}V_{cc} = t_c$
the o/p is high and is given by,

$$t_c = 0.69(R_A + R_B)C$$

Time during which C discharges from $\frac{2}{3}V_{cc}$ to $\frac{1}{3}V_{cc} = t_d$
the o/p is low and is given by,

$$t_d = 0.69(R_B)C$$

Total period of the o/p waveform is,

$$T = t_c + t_d = 0.69(R_A + 2R_B)C$$

So, freq. of oscillation, $f_o = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C}$ — (A)

(A) shows that f_o is independent of the supply voltage V_{cc} .

Duty cycle = Ratio of time t_c during which the o/p is high to the total time period T .

$$\% \text{ Duty cycle} = \frac{t_c}{T} \times 100 = \frac{R_A + R_B}{R_A + 2R_B} (100) \%$$