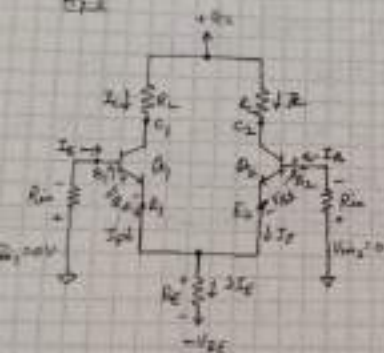


Since the transistors are identical, β of the signal sources are equal and therefore the voltage drop across them can be taken as negligible. Since the transistors are matched and biased, the operating point obtained for one transistor is same for the other. The dc equivalent circuit for all the four configurations is same, therefore the dc analysis done later applies for all the configurations.

Revise the circuit of Fig 2 by labelling the two input voltages to give -

Ex 2



- Operating from $V_{BE1} = V_{BE2}$ for both transistors
- $I_{B1} = I_{B2}$ for all time
- Voltage drop across R_B negligible
- $V_{BE1} = 0.7V$ for Q_1
 $= 0.7V$ for Q_2
- $I_C = I_E$

Applying Kirchhoff's Voltage Law for BE circuit for Transistor Q_1 ,

$$-R_B I_B - V_{BE} - R_E (2I_E) + V_{EE} = 0 \quad (1)$$

Put $I_B = I_C / \beta$ in Eq. (1) assuming $I_C = I_E$

$$-R_B \frac{I_E}{\beta} - V_{BE} - 2R_E I_E + V_{EE} = 0$$

$$-I_E \left(\frac{R_B}{\beta} + 2R_E \right) = -(V_{EE} - V_{BE})$$

- When we use only one input signal : Single input
- When the output is taken between two collectors :
balanced output
- When the output is taken from one of the collectors
w.r.t. ground : unbalanced output

In analyzing difference amplifiers, 2-parameters
are used because they are

- simpler, more straightforward
- unlike h-parameters, no need to manipulate h-parameters at operating points.
- easy to describe equations, etc.


Balanced Output :

The two collectors of the two transistors are at the same dc voltages w.r.t. the ground.

Unbalanced Output :

The collector at which the output is measured is at a definite dc voltage even when no input is given.

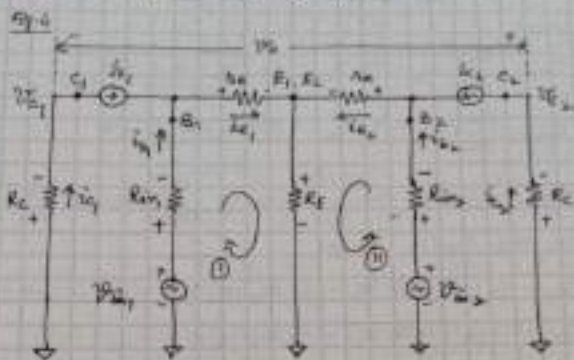The DC voltage sources are started out, and transistors are replaced by their T-equivalent models based on r-parameter. Equivalent circuit (AC) of Fig. 3.



Voltage Gain

Ans: 1. Two identical common-emitter circuit with matched transistors, etc., therefore


$$I_{B1} = I_{B2} = I_B \text{ and}$$

$$R_{E1} = R_{E2} = R_E$$

2. Because of the common-emitter configurations, the voltages at the collectors are shown to be 180° out of phase with that of V_{be1} and V_{be2} .
3. Collector C_2 is assumed to be more positive w.r.t. C_1 , even though ϕ both are negative w.r.t. the ground.

A differential amplifier is the basic building block of operational amplifiers. Consider two identical emitter-biased transistor circuits.


Fig. 1

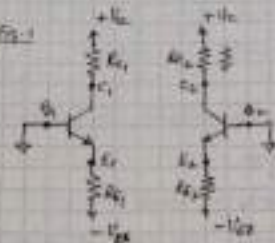

- The transistors have same characteristics
- $R_{C1} = R_{C2}$, $R_{E1} = R_{E2}$
- $|V_{C1}| = |V_{C2}|$ and are measured w.r.t. ground.

Reconnect the above circuit with $R_C = R_{C1} = R_{C2}$ & $R_E = R_{E1} = R_{E2}$ and common supply voltages as shown below:

Fig. 2

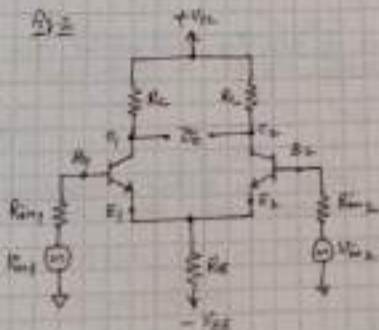

- Differential amplifier amplifies difference between input signals V_{i1} & V_{i2}
- V_o is the output voltage
- R_{i1} and R_{i2} are internal resistances of the signal sources and are equal, $R_{i1} = R_{i2}$
- This circuit is dual input, balanced output diff amp

FOUR Configurations of differential (difference) amplifier are:

1. Dual-input, balanced output
2. Dual-input, unbalanced output
3. Single-input, balanced output
4. Single-input, unbalanced output

$$I_E = \frac{V_{EE} - V_{BE}}{2R_E} \quad \left| \quad 2R_E \gg \frac{R_B}{\beta} \right. \quad (3)$$

It is clear that I_E is set up by R_E and is not dependent upon R_B .

For V_{CE} , assuming voltage across R_E to be negligible, the emitter R_E is at $-V_{EE}$ if $I_C \approx I_E$. Considering base-collector circuit, the collector R_C is at voltage

$$V_C = V_{CC} - R_C I_C$$

$$\text{And } V_{CE} = V_C - V_E \\ = V_{CC} - R_C I_C - (-V_{EE})$$

$$V_{CE} = V_{CC} - R_C I_C + V_{EE} \quad (4)$$

The operating point for the transistor A, is (I_C, V_{CE}) , as I_C and V_{CE} are given by equations (3) to (4).

This operating point for any n both the transistors is written as

$$I_{CQ} = I_E$$

$$V_{CEQ} = V_{CE}$$

$$i_{e2} = \frac{\begin{vmatrix} R_E & v_{in2} \\ r_e + R_E & R_E \end{vmatrix}}{\begin{vmatrix} r_e + R_E & R_E \\ R_E & r_e + R_E \end{vmatrix}}$$

$$= \frac{(r_e + R_E)v_{in2} - R_E v_{in1}}{[(r_e + R_E)^2 - R_E^2]} \rightarrow R_E (r_e + 2R_E)$$

The output voltage =

$$v_o = v_{e2} - v_{e1}$$

$$= -R_E i_{e2} - (-R_E i_{e1})$$

$$= R_E i_{e1} - R_E i_{e2}$$

$$= R_E (i_{e1} - i_{e2})$$

Since $i_e = i_o$

Putting (1) & (2) in (4),

$$v_o = R_E \left[\frac{(r_e + R_E)v_{in1} - R_E v_{in2}}{(r_e + R_E)^2 - R_E^2} - \frac{(r_e + R_E)v_{in2} - R_E v_{in1}}{(r_e + R_E)^2 - R_E^2} \right]$$

$$= R_E \left[\frac{(r_e + R_E)(v_{in1} - v_{in2}) + R_E(v_{in1} - v_{in2})}{(r_e + R_E)^2 - R_E^2} \right]$$

$$= R_E \left[\frac{(r_e + 2R_E)(v_{in1} - v_{in2})}{(r_e + R_E)^2 - R_E^2} \right]$$

$$= R_E \left[\frac{(r_e + 2R_E)(v_{in1} - v_{in2})}{r_e^2 + R_E^2 + 2r_e R_E - R_E^2} \right]$$

$$= R_E \left[\frac{(r_e + 2R_E)(v_{in1} - v_{in2})}{r_e(r_e + 2R_E)} \right]$$

$$V_{in1} - R_{in1} i_{o1} - R_L i_{o1} - R_E (i_{o1} + i_{o2}) = 0$$

Substituting in above equations

$$i_{o1} = \frac{V_{in1}}{R_{in1}} \quad \text{and} \quad i_{o2} = \frac{V_{in2}}{R_{in2}}$$

we get

$$V_{in1} - \frac{R_{in1}}{R_{in1}} i_{o1} - R_L i_{o1} - R_E (i_{o1} + i_{o2}) = 0$$

$$V_{in2} - \frac{R_{in2}}{R_{in2}} i_{o2} - R_L i_{o2} - R_E (i_{o1} + i_{o2}) = 0$$

Neglect second term because $\frac{R_{in1}}{R_{in1}}$ and $\frac{R_{in2}}{R_{in2}}$ are very small. We get

$$V_{in1} - R_L i_{o1} - R_E i_{o1} - R_E i_{o2} = 0$$

$$V_{in2} - R_L i_{o2} - R_E i_{o1} - R_E i_{o2} = 0$$

Rearranging, we get

$$(R_L + R_E) i_{o1} + R_E i_{o2} = V_{in1} \tag{7}$$

$$R_E i_{o1} + (R_L + R_E) i_{o2} = V_{in2} \tag{8}$$

Using Cramer's rule to solve equations (7) and (8) simultaneously for i_{o1} and i_{o2} :

$$\begin{vmatrix} V_{in1} & R_E \\ V_{in2} & R_L + R_E \end{vmatrix}$$

$$i_{o1} = \frac{\begin{vmatrix} V_{in1} & R_E \\ V_{in2} & R_L + R_E \end{vmatrix}}{\begin{vmatrix} R_L + R_E & R_E \\ R_E & R_L + R_E \end{vmatrix}} \tag{9}$$

$$= \frac{(R_L + R_E) V_{in1} - R_E V_{in2}}{(R_L + R_E)^2 - R_E^2} \tag{10}$$

resistance measured at either input terminal with the other terminal grounded with R_1 , and this neglected as they are very small, the differential input resistance is

$$R_{i1} = \left. \frac{V_{in1}}{I_{in1}} \right|_{V_{in2}=0} = \left. \frac{V_{in1}}{I_{in1}/\beta_{ac}} \right|_{V_{in2}=0} \quad (19)$$

$$R_{i2} = \left. \frac{V_{in2}}{I_{in2}} \right|_{V_{in1}=0} = \left. \frac{V_{in2}}{I_{in2}/\beta_{ac}} \right|_{V_{in1}=0} \quad (20)$$

Substituting the value of V_{in1} from eq(19) in eq(20), we get

$$\begin{aligned} R_{i2} &= \frac{\beta_{ac} V_{in1}}{(r_e + R_E) I_{in1} - R_E (0)} \\ &= \frac{\beta_{ac} V_{in1}}{(r_e + R_E) I_{in1}} \rightarrow r_e^2 + R_E^2 + 2r_e R_E \\ &= \frac{\beta_{ac} V_{in1}}{r_e^2 + 2r_e R_E} \rightarrow r_e (r_e + 2R_E) \\ &= \frac{\beta_{ac} V_{in1} r_e (r_e + 2R_E)}{(r_e + R_E) I_{in1}} \end{aligned}$$

generally $R_E \gg r_e$, therefore r_e can be neglected in the bracketed terms.


$$R_{i2} = \frac{\beta_{ac} r_e \cdot 2R_E}{R_E}$$

$$R_{i2} = 2 \beta_{ac} r_e \quad (21)$$

INTERNAL ARCHITECTURE (Block Diagram) OP AMP


It is a direct coupled high gain amplifier consisting of one or more differential amplifiers followed by a level shifter and a push-out or push-out complementary symmetry pair. It is a single chip IC.

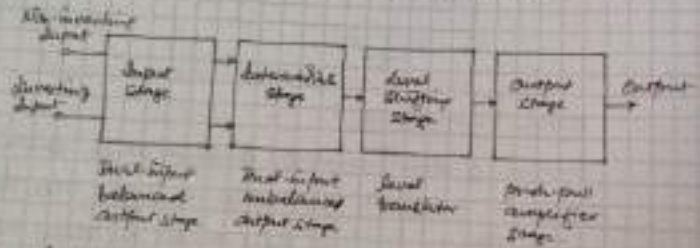Available device, used for initially for mathematical operations, hence its name operational amplifier. Apart from mathematical operations, op amps are used in amplifier, oscillators, filters, comparators, regulators and other circuits. Block diagram:



Input stage establishes the input resistance of the op-amp. The output stage, a push-out complementary-symmetry amplifier, increases the output voltage swing and raises the current supplying capability of the op-amp. Output stage provides low output resistance.

SYMBOL

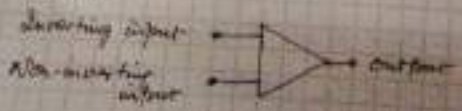

• difference in two input signals

The voltage-gain of dual input, balanced output differential amplifier is


$$A_d = \frac{V_o}{V_{id}} = \frac{R_c}{r_e} \quad (18)$$

Thus a differential amplifier amplifies the difference between two input signals.

- This equation is identical to that for voltage-gain for common-emitter amplifier, and
- is independent of β .

Input and output waveforms of dual-input, balanced-output differential amplifier is as shown in Fig. 5

Fig. 5

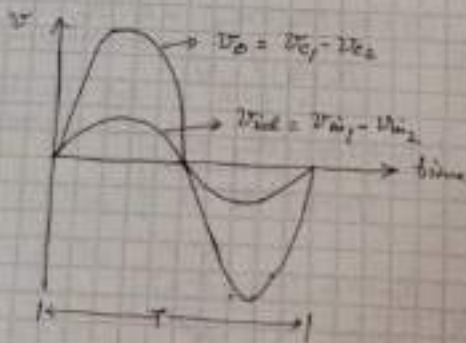

$$R_{i2} = \frac{\beta_{ac} V_{i2}}{(V_c + R_c) V_{i2} - R_c V_c}$$

$$R_{i2} = \frac{\beta_{ac} V_{i2} V_c (V_c + 2R_c)}{(V_c + R_c) V_{i2}}$$

$$= \frac{\beta_{ac} V_c (V_c + 2R_c)}{V_c} \quad | \quad R_c \gg V_c$$

$$R_{i2} = 2\beta_{ac} R_c \quad (22)$$

From eqs. (21) and (22), we conclude that

$$R_{i1} = R_{i2} \quad (23)$$

Output resistance

By definition, the output resistance is the equivalent resistance measured at either collector w.r.t. ground.

From Fig. 4, it is clear that


$$R_{o1} = R_{o2} = R_c \quad (24)$$

Identifying & Non-inverting inputs

From Fig. 2 and eq. (15), it is clear that V_{i1} , if acting alone, decides the output polarity. If V_{i1} is +ve, V_o is +ve and if V_{i1} is -ve, V_o is -ve. Therefore V_{i1} is called non-inverting input and base B_1 is called the inverting input terminal.

Similarly if V_{i2} is acting alone, the polarity of the V_o is opposite to that of V_{i2} . That is if V_{i2} is +ve, V_o is -ve and if V_{i2} is -ve, V_o is +ve. Therefore V_{i2} is called inverting input and base B_2 is called non-inverting input terminal.

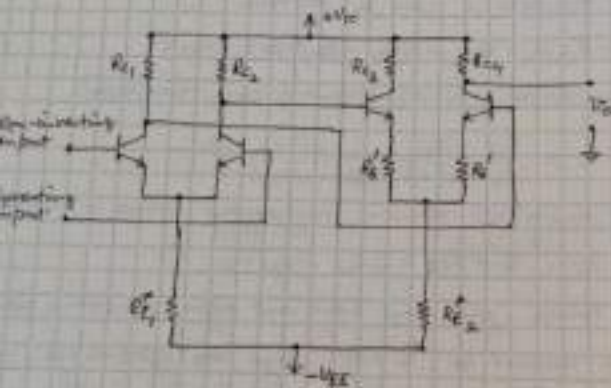second a pair. The stage that stage is a dual-type, balanced input differential amplifier. Second stage is another differential amplifier driven by the output of the first stage. A single ended unbalanced output is taken from the second stage. Transistor arrays (A3052 or LM3146) offer electrical and thermal matching, compensation and ease of handling.



$$V_{in} = -V_{in} \quad (V_{in} + V_{in} = 2V_{in})$$

$$= R_c \frac{R_c V_{in} - R_c V_{in}}{2R_c R_c} \quad | = R_c V_{in}$$

$$= R_c \frac{R_c (V_{in1} - V_{in2})}{2R_c R_c}$$

$$= \frac{R_c}{2R_c} (V_{in1} - V_{in2}) = \frac{R_c}{2R_c} V_{in}$$

$$A_d = \frac{V_o}{V_{in}} = \frac{R_c}{2R_c} \quad (20)$$

Comparing this eq. (20) with eq. (19), we conclude that the voltage gain of dual input unbalanced output difference amplifier is half of that of dual input balanced output difference amplifier.


Since the input resistances do not depend how the output is taken, therefore from eqs. (19), (20) and (21),

$$R_{i1} = R_{i2} = 2R_c \quad (23)$$

The output resistance is the resistance seen at C_2 ,

$$R_o = R_c \quad (24)$$

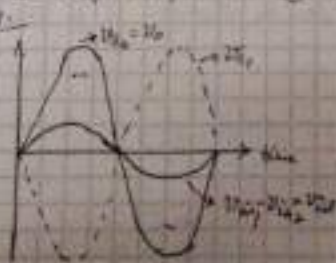The output input waveforms are shown in Fig. 7.




In this case the voltage v_{in} is also present at the output terminals. To reduce this undesired voltage to zero, this amplifier is followed by a level translator.


3. Dual-Input, Unbalanced Output Case

The differential amplifier of Fig. 2 is redrawn with output taken from the collector C_2 only.

Fig. 3

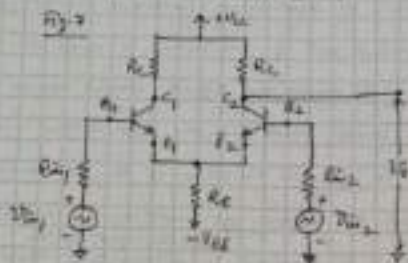

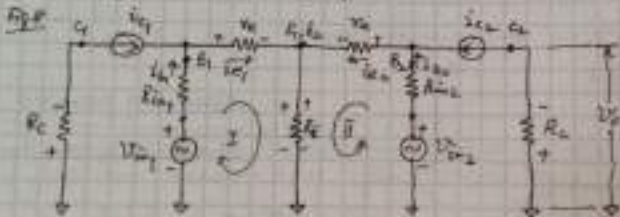An equivalent circuit of Fig. 3 is redrawn with output taken from collector C_2 only.




Since the above two circuits are same as that of Figs. (a) and (b), except that the output is taken only from collector C_2 , the Kirchhoff's voltage equations for loops I and II are same as eqs. (a) & (b). Therefore, i_{C1} and i_{C2} equations are also same as eqs. (a) and (b).

The output voltage V_o is

$$\begin{aligned} V_o = V_{C2} &= -R_C i_{C2} \\ &= -R_C i_{C2} \quad i_{C2} = i_{C2} \quad (27) \end{aligned}$$

Substituting for i_{C2} from eq. (26) in eq. (27), we get

The ability to suppress undesired disturbances, pick-ups, noise, etc. is called common-mode rejection. The desired signal is an important characteristic of dual input, balanced output differential amplifier. When matched pair of transistors is used in the differential amplifier, the undesired signals would appear as common to both the bases, and therefore such output would be essentially zero. The effective rejection of the common mode signal depends upon the degree of matching of transistors. When the same signal is applied to both the inputs of the differential amplifier, the differential amplifier is said to be working in common-mode configuration. The CMRR is defined as the ability to reject common-mode signal.

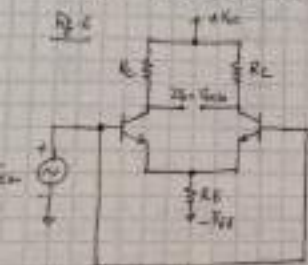

$$CMRR = \frac{\text{Differential gain, } A_d}{\text{Common-mode gain, } A_{cm}} \quad (25)$$

where

$$A_{cm} = \frac{V_{ocm}}{V_{cm}} \quad (26)$$

V_{cm} is common to both the terminals.

Ideally $A_{cm} = 0$, (i.e. $V_{ocm} = 0$). Thus, ideally, $CMRR = \infty$. The differential amplifiers, with higher $CMRR$ should be used, since it is better able to reject common-mode signals.

$$V_{O2} = 20 \text{ mV pp at } 1 \text{ kHz}$$

$$\begin{aligned} V_o &= \frac{R_c}{R_e} (V_{in1} - V_{O2}) \\ &= 86.96 (50 \text{ mV} - 20 \text{ mV}) \\ &= 2.61 \text{ V pp} \end{aligned}$$

Maximum peak-to-peak variation

$$\begin{aligned} V_{Rc} &= I_C R_c \\ &= 0.988 \text{ mA} \times 2.2 \text{ k}\Omega \\ &= 2.17 \text{ V} < V_{CE} = 8.53 \text{ V} \end{aligned}$$

Maximum change in Voltage at collector is

$$\pm 2.17 \rightarrow 4.34 \text{ V pp}$$

In Dual-input, balanced output case

$$\text{Maximum change is } 2 \times 4.34 = 8.68 \text{ V pp}$$

In Dual-input, unbalanced output case

$$\text{Maximum change is } 4.34 \text{ V pp}$$

$$v_{i1} = +10V, \quad v_{i2} = -10V, \quad R_{in} = R_{in} = 100, \quad v_{o1} = v_{o2} = 20V$$

For dual-input, balanced input differential amplifier:

$$I_{i1} = I_{i2} = I_{i2} = I_{i1}, \quad \text{and} \quad (ii) \quad R_{i1} = R_{i2}$$

$$(i) \quad I_{i1} = I_{i2} = \frac{V_{i1} - V_{i2}}{2R_e + R_{in}/\beta} = \frac{10 - (-10)}{2 \times 100 + 100/\beta} = 0.988 \text{ mA}$$

$$\begin{aligned} V_{o1} &= V_{i1} + V_{i2} - R_e I_{i1} \\ &= 10 + 0.10 - (2000)(0.988) \text{ mV} \\ &= 8.54 \text{ V} \end{aligned}$$

(ii) AC emitter resistance

$$r_e = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{0.988 \text{ mA}} = 25.3 \Omega$$

$$\begin{aligned} \text{Voltage Gain } A_v &= \frac{V_o}{V_{in}} = \frac{R_c}{r_e} \\ &= \frac{2200}{25.3} = 86.96 \end{aligned}$$

$$\begin{aligned} (iii) \quad R_{i1} = R_{i2} &= 2\beta R_e r_e = 2 \times 100 \times 25.3 = 5060 \\ &= 5.06 \text{ k}\Omega \end{aligned}$$

$$R_{o1} = R_{o2} = 2.2 \text{ k}\Omega$$

For dual-input unbalanced output case

$$A_d = \frac{R_c}{2r_e} = \frac{2200}{2 \times 25.3} = 42.48$$


For single-input balanced output gain is same as that in case of dual-input balanced output.

When the dc current is changed the base voltage AC resistance is closely approximated by $R_e = V_T/I_E$, where V_T = thermal voltage = kT/q and I_E is emitter current. At $T = 300 \text{ K}$, $V_T = 0.026 \text{ V}$, so we can say $r_e = \frac{25 \text{ mV}}{I_E}$.

Begin

CASCDED DIFFERENTIAL AMPLIFIER

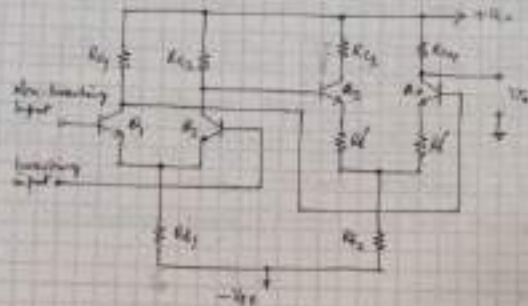Two stages case. First stage load is not balanced output stage and second is unbalanced output stage. Direct coupling.



LEVEL TRANSLATOR

Because of direct coupling, the level at the outputs rises from stage to stage. This increase in dc level tends to shift the operating point of the succeeding stages. Therefore, it limits the output voltage swing and may even distort the output signal. A final stage is included which brings down the dc level at the second stage to give 0V dc. Such a stage is known as level translator which is shown in the figure. Proper selection of R_1 and R_2 produces 0V at the junction of R_1 and R_2 .



as level translator which is shown in the figure. Proper selection of R_1 and R_2 produces 0V at the junction of R_1 and R_2 .