

CHAPTER 7:
SEQUENTIAL CIRCUITS –
FLIP-FLOPS, REGISTERS,
AND COUNTERS

What will we learn?

2

- Logic circuits that can store information
 - Latches, which store *a single bit*
 - Flip-Flops, which store *a single bit*
 - Registers, which store *multiple bits*
- Shift registers
- Counters
- Design Examples

Sequential Circuits

3


- Combinational Circuits
 - circuits without feedback
 - output = f (current inputs)

- Sequential Circuits
 - circuits with feedback
 - output = f (current inputs, past inputs, past outputs)
 - how can we feed the past inputs and outputs into the circuits?
 - basis for building “memory” into logic circuits

Circuits with feedback


4

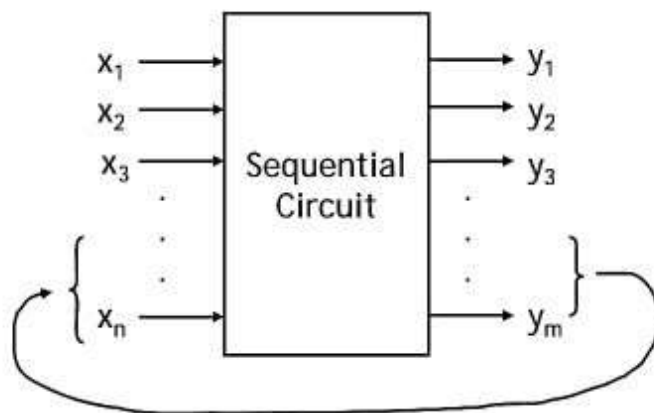- How to control feedback?
 - what stops values from cycling around endlessly



Control of an alarm system


5

 

- the simplest case of a sequential circuit
 - Alarm is on when the sensor generates the “Set” signal in response to some undesirable events
 - Once the alarm is on, it can only be turned off manually through a reset button
- Memory is needed to remember that the alarm has to be active until the reset signal arrives

A simple memory element

 
- The most rudimentary memory element
 - Two inverters form a static memory cell
 - Assume $A=0$ and $B=1$, then the below circuit will maintain these values indefinitely (as long as it has power applied)
 - The state is defined by the value of the memory cell
 - Two states



- How to get a new value into the memory cell?
 - selectively break feedback path
 - load new value into cell

A controlled memory element

7

 


A memory element with NOR gates


8

- Construct a memory cell using ordinary logic gates
 - Two NOR gates are connected in cross-coupled style
 - Basic Latch

- Two inputs
 - Set
 - Reset

 


A basic latch built with NOR gates

 

(a) Circuit

S	R	Q _a	Q _b
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	0	0

 (b) Truth table or *characteristic table*




(c) Timing diagram


There will be an oscillation

Timing Waveform

10

 

Timing Waveform

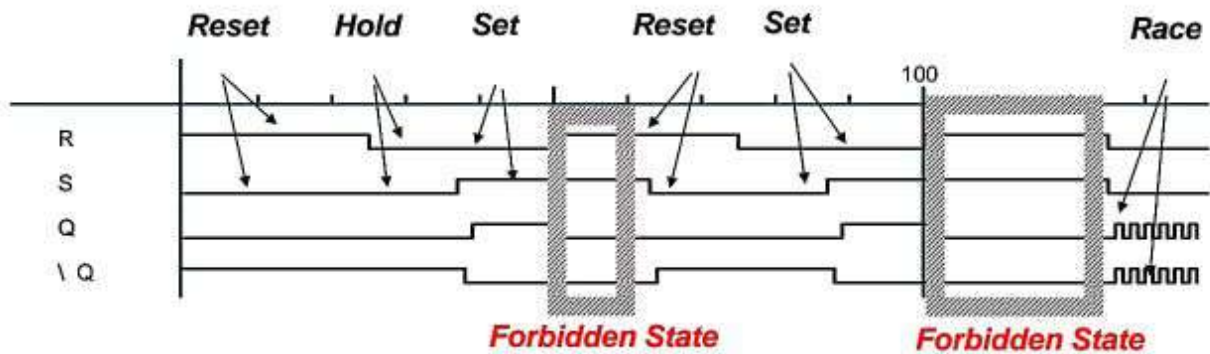

State Behavior of R-S Latch

11

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	unstable


**Truth Table Summary
of R-S Latch Behavior**



Theoretical R-S Latch State Diagram


12

 - State Diagram
 - ▣ state: possible values
 - ▣ transitions: changes based on inputs



Observed R-S Latch Behavior

13

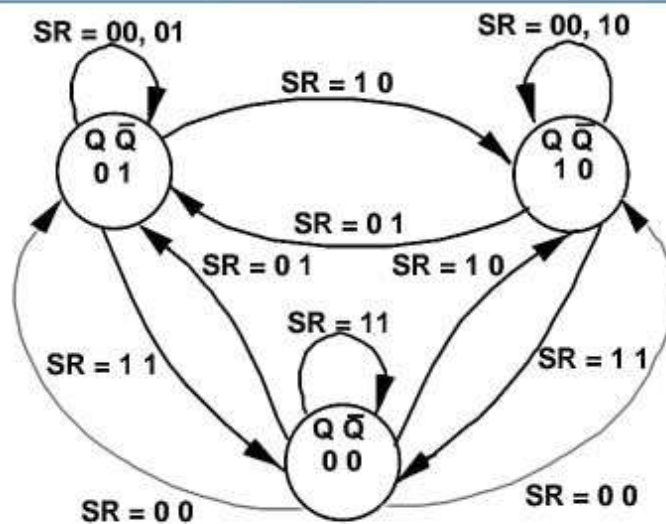

Very difficult to observe R-S Latch in the 1-1 state

Ambiguously returns to state 0-1 or 1-0


A so-called "race condition"

R-S Latch Analysis

Truth Table:
Next State = F(S, R, Current State)

R-S Latch Revisited

S	R	Q_t	Q_+	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset 0
0	1	1	0	
1	0	0	1	set 1
1	0	1	1	
1	1	0	x	not allowed
1	1	1	x	

 

Derived K-Map:

		S			
		00	01	11	10
Q(t)	0	0	0	X	1
	1	1	0	X	1
		R			

Characteristic Equation:

$$Q_+ = S + \bar{R} Q_t$$

Problems of R-S Latch



15

- *The slightest glitch on R or S* could cause change in value stored
 - R-S Latch has transparent outputs
 - Transparent outputs : when the memory element's outputs immediately change in response to input changes

- Want to control *when R and S inputs have effect on value stored*
 - Enable Signal (or clock signal)
 - R and S inputs are active *only when Enable = 1*
 - Gated Latches or Level sensitive latches


Gated SR latch

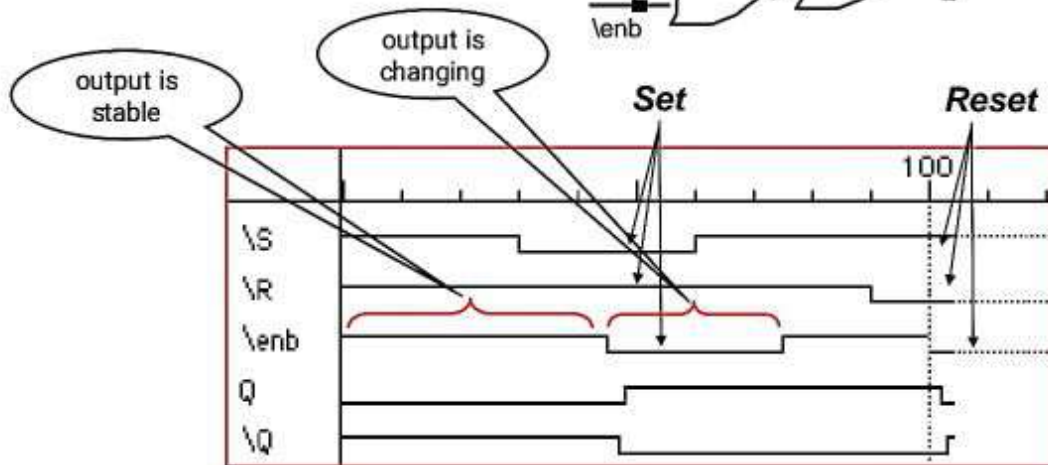 - *Control when R and S inputs matters*
 - the latch can be modified to respond to the input signal S and R only when Enable = 1



Gated SR Latch


17

 


clk	S	R	Q(r+1)
0	x	x	Q(r) (no change)
1	0	0	Q(r) (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(a) Circuit

(b) Characteristic table

 


(c) Timing diagram

 

(d) Graphical symbol

Gated SR latch with NAND gates

18

 

Problems of the Gated S/R Latches

19


- 1. Forbidden State and Race condition
 - How to eliminate the forbidden state and race condition
 - When $S=R=1$, $Q=\bar{Q}=0$ (forbidden state)
 - Oscillation (Race condition)
 - D-type Latch
 - JK-Latch (toggling)
 - The output toggles forever when $J=K=1$

- 2. When cascading level-sensitive Latches
 - Master/Slave F/F's
 - Edge-triggered F/F's

 1. How to eliminate the forbidden state?

□ Gated D-latch


- eliminate the troublesome situation where $S=R=1$




(a) Circuit

Clk	D	$Q(z+1)$
0	x	$Q(z)$
1	0	0
1	1	1

(b) Characteristic table

 

(c) Graphical symbol

 

(d) Timing diagram

How to eliminate the forbidden state? cont'd


21

Idea: use output feedback to guarantee that R and S are never both one

J, K both one yields toggle

J-K Latch

J(t)	K(t)	Q(t)	Q+	
0	0	0	0	hold
0	0	1	1	
0	1	0	0	reset 0
0	1	1	0	
1	0	0	1	set 1
1	0	1	1	
1	1	0	1	toggle
1	1	1	0	

 


Characteristic Equation:

$$Q+ = Q \bar{K} + \bar{Q} J$$

J-K Latch: Toggles forever in the toggle mode

22

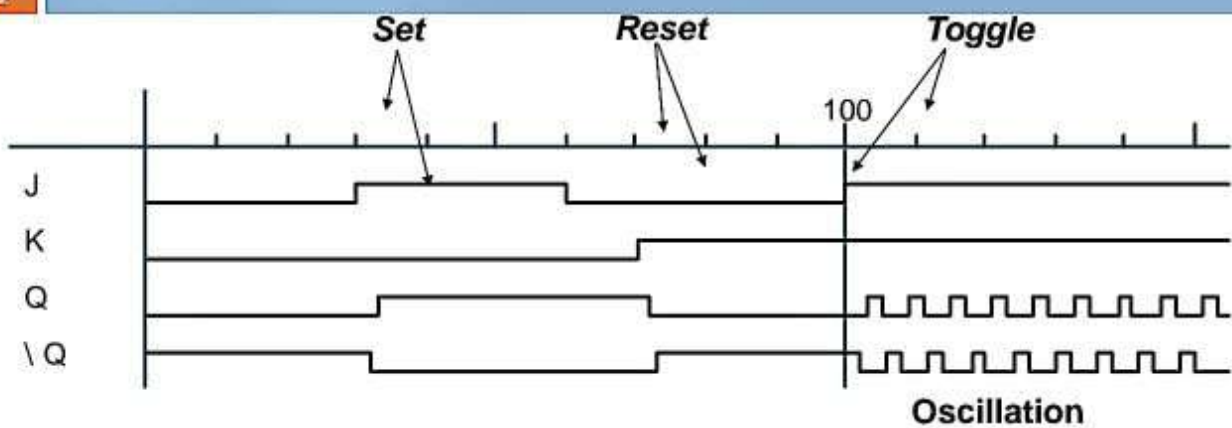

Toggle Correctness: Single State change per clocking event

Solution: Master/Slave Flipflop