

# Lecture -02


Paper Name:	Analog System and Application
Teacher Name:	Lalit Kumar
Course & Semester:	B.Sc (H) Physics, 4 <sup>th</sup> Semester, Section A
Department:	Physics

## Reciprocal network.

→ A two port network is said to be reciprocal network, if the ratio of the excitation at one port to the response at other port is same, if the excitation and the response are interchange.

Condition of Reciprocity,  $[h_{12} = -h_{21}]$

Proof:

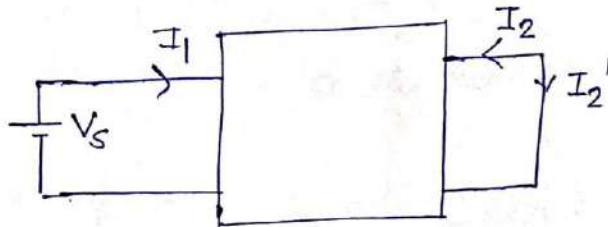

So here  $V_1 = V_s$ , and  $V_2 = 0$ ,


$$I_2 = -I_2'$$

from  $V_1 = h_{11}I_1 + h_{12}V_2 \Rightarrow V_s = h_{11}I_1$

$$I_2 = h_{21}I_1 + h_{22}V_2 \Rightarrow -I_2' = h_{21}I_1$$

$$\Rightarrow \frac{V_s}{-I_2'} = \frac{h_{11}}{h_{21}} \Rightarrow \left[ \frac{V_s}{I_2'} = -\frac{h_{11}}{h_{21}} \right] \text{--- ①}$$

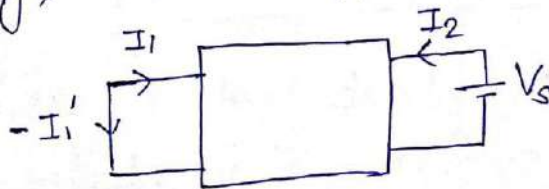Similarly, voltage  $V_s$  is applied at port 2,



so here  $V_2 = V_s, V_1 = 0, I_1 = -I_1'$

Putting this value in eqn.

$$V_1 = h_{11}I_1 + h_{12}V_2 \Rightarrow 0 = -h_{11}I_1' + h_{12}V_s \Rightarrow \frac{V_s}{I_1'} = \frac{h_{11}}{h_{12}} \quad \text{--- (2)}$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

Now if the network is reciprocal then equation (1) and eqn (2) should be equal. or  $\frac{h_{11}}{h_{12}} = -\frac{h_{11}}{h_{21}} \Rightarrow [h_{21} = -h_{12}]$


from (1) & (2)

$$\frac{V_s}{I_1'} = \frac{V_s}{I_2} \Rightarrow \frac{h_{11}}{h_{12}} = -\frac{h_{11}}{h_{21}} \Rightarrow (h_{21} = -h_{12})$$

So the network is Reciprocal.

§ Performance of a linear circuit in terms of h-parameters.

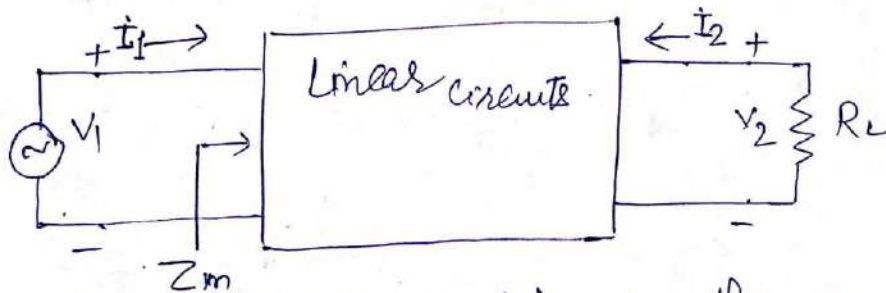We have a linear two port network, has a set of h-parameters.



Now, here we shall develop the formula for Input Impedance  $Z_{in}$ , Current gain  $A_i$ , Voltage gain  $A_v$ , etc in terms of h-parameters

## 1) Input Impedance $Z_{in}$ :

The input impedance  $Z_{in}$  of a linear circuit is defined as  $Z_{in} = \frac{V_1}{I_1}$  — (1)

from the h-parameter equation we know

$$V_1 = h_{11}I_1 + h_{12}V_2 \text{ — (2)}$$

from (1) & (2)  $Z_{in} = \frac{h_{11}I_1 + h_{12}V_2}{I_1} = h_{11} + \frac{h_{12}V_2}{I_1}$  — (3)

Now,  $I_2 = h_{21}I_1 + h_{22}V_2$  — (4)

from two port network circuit (As in fig)

$$I_2 = -\frac{V_2}{R_L} \text{ — (5)}$$

(-ve sign indicates that actual current is flowing opposite to the conventional current direction)

from equation (4) and (5)

$$\Rightarrow -\frac{V_2}{R_L} = h_{21}I_1 + h_{22}V_2$$

$$\Rightarrow -h_{21}I_1 = h_{22}V_2 + \frac{V_2}{R_L} = \left(h_{22} + \frac{1}{R_L}\right)V_2$$

$$\Rightarrow \frac{V_2}{I_1} = \frac{-h_{21}}{\left(h_{22} + \frac{1}{R_L}\right)} \text{ — (6)}$$

put equation (6) in equation (3)

$$\left\{ Z_{in} = h_{11} - \frac{h_{12} h_{21}}{h_{22} + \frac{1}{R_L}} \right\} \text{ This is the expression for input impedance of two port network in terms of } h\text{-parameters}$$

(2) Current gain  $A_i \Rightarrow$  For the two port network the current gain is defined as.

$$A_i = \frac{I_2}{I_1} \quad \text{--- (7)}$$

We know for two port network.

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (8)}$$

$$\& V_2 = -I_2 R_L$$

$$\therefore I_2 = h_{21} I_1 - h_{22} I_2 R_L$$

$$I_2 (1 + h_{22} R_L) = h_{21} I_1$$

$$\left[ A_i = \frac{I_2}{I_1} = \frac{h_{21}}{(1 + h_{22} R_L)} \right] \quad \text{--- (9)}$$

This is the expression current gain of two port

network in terms of  $h$ -parameters.

In actual  $I_2 = -I_2'$

$$\therefore \left[ A_i = - \frac{h_{21}}{(1 + h_{22} R_L)} \right]$$

3) Voltage gain  $A_v \rightarrow$

$$A_v = \frac{V_2}{V_1} \quad \text{--- (10)}$$

We know  $V_1 = I_1 Z_{in}$

$$\therefore A_v = \frac{V_2}{I_1 Z_{in}} \rightarrow \frac{V_2}{I_1} \quad \text{--- (11)}$$

from equation (6)


$$\frac{V_2}{I_1} = \frac{-h_{21}}{(h_{22} + \frac{1}{R_L})} \quad \text{--- (12)}$$

Put eqn (12) in eqn (11)

$$\left[ A_v = \frac{-h_{21}}{Z_{in} \left[ (h_{22} + \frac{1}{R_L}) \right]} \right] \quad \text{Voltage gain of two port network in terms of } h\text{-parameters}$$

④ Output Impedance  $Z_{out} \rightarrow$  To find out the

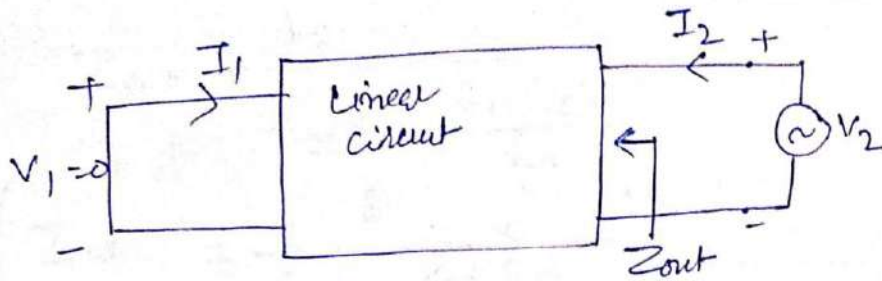$Z_{out}$ , we require to set  $V_1 = 0$ , and connect a current generator of voltage  $V_2$  at output terminals. the new modified circuit will be



then  $Z_{out} = \frac{V_2}{I_2}$  — (14)

from h-parameter equations for two port network

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \text{--- (15)}$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \text{--- (16)}$$

with  $V_1 = 0$  (input) and applying KVL to the input ckt  
from (15)  $0 = h_{11}I_1 + h_{12}V_2$

$$I_1 = -\frac{h_{12}}{h_{11}}V_2 \quad \text{--- (17)}$$

from (16)  $I_2 = h_{21}I_1 + h_{22}V_2$

Put  $I_1$  from (17)  $I_2 = -h_{21}\left(\frac{h_{12}}{h_{11}}\right)V_2 + h_{22}V_2$

$$I_2 = -\frac{h_{21}h_{12}V_2}{h_{11}} + h_{22}V_2 \quad \text{--- (18)}$$



Put  $I_2$  from eqn (18) into (14)

$$Z_{out} = \frac{V_2}{h_{22}V_2 - \frac{h_{21}h_{12}V_2}{h_{11}}}$$

$$\left[ Z_{out} = \frac{1}{h_{22} - \frac{h_{21}h_{12}}{h_{11}}} \right] \text{--- (19)}$$

\* Numerical Problems \*

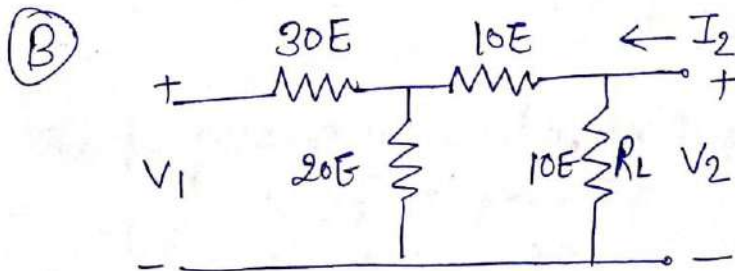
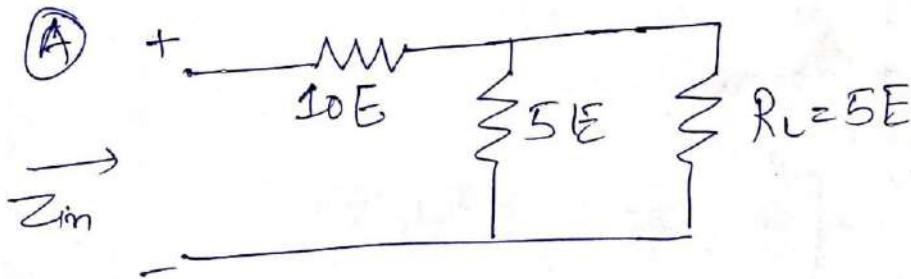
Find the (1) Input Impedance  
(2) Voltage gain for the circuits





## Transistor as a two port network

### § C-E amplifier:

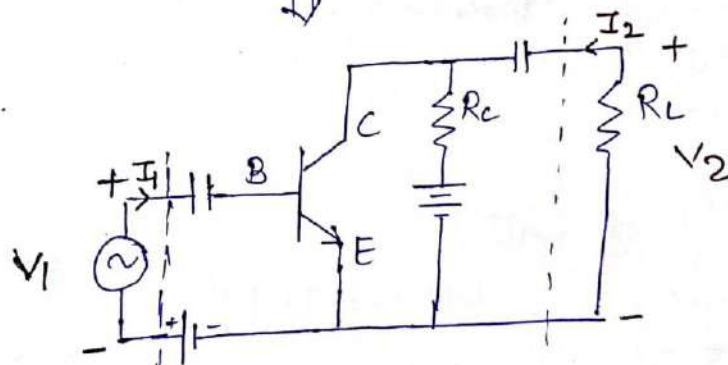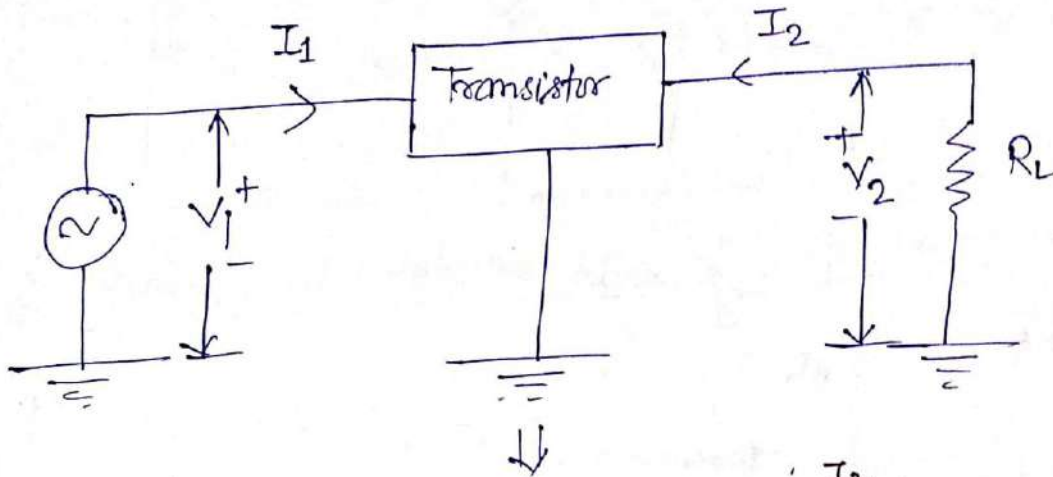

The  $h$ -parameters equations for two port network (Transistor),


$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2.$$

⇒ Nomenclature for transistor  $h$ -parameters (in CE)


$$h_{11} = h_{ie}, \quad h_{12} = h_{re}, \quad h_{21} = h_{fe}, \quad h_{22} = h_{oe}$$

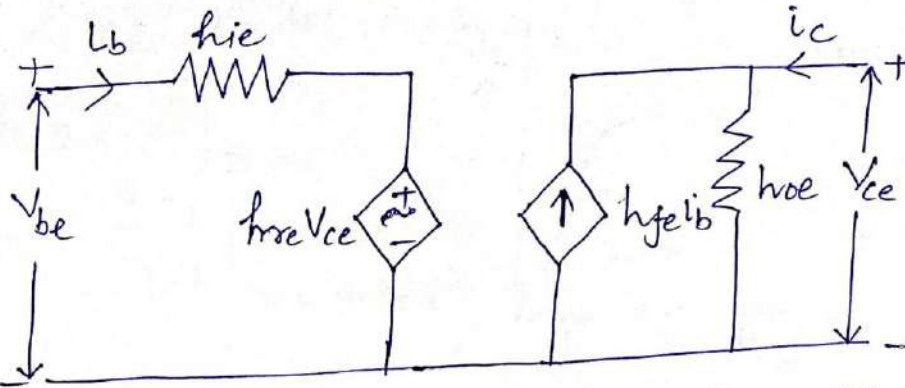⇒ Common emitter equivalent circuit in h-parameters




§ Graphical determination of H-Parameters (For CE)

$$1) h_{11} = h_{ie} = \left. \frac{\Delta V_{BE}}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

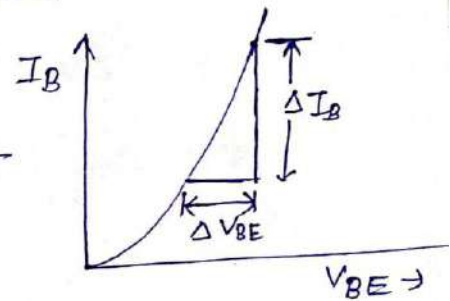


$$2) h_{22} = h_{re} = \left. \frac{\Delta V_{BE}}{\Delta V_{CE}} \right|_{I_B = \text{constant}}$$

$$\Delta V_{CE} = V_{CE2} - V_{CE1}$$

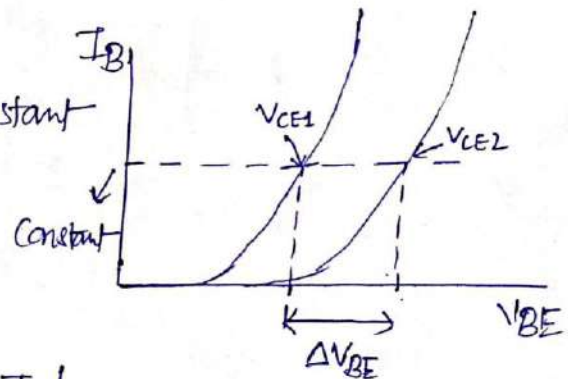

$$3) h_{21} = h_{fe} = \left. \frac{I_2}{I_1} \right|_{V_2 = 0} = \beta$$

$$= \left. \frac{\Delta I_c}{\Delta I_B} \right|_{V_{CE} = \text{const}}$$

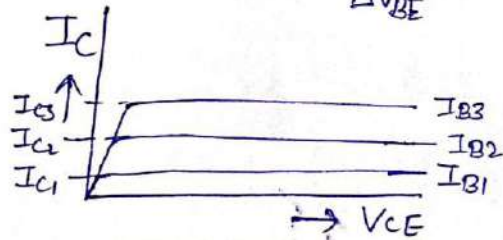


$$\Delta I_c = I_{c2} - I_{c1}$$

$$\Delta I_B = I_{B2} - I_{B1}$$

$$4) h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

$$h_{22} = \left. \frac{\Delta I_c}{\Delta V_{CE}} \right|_{I_B = \text{constant}}$$

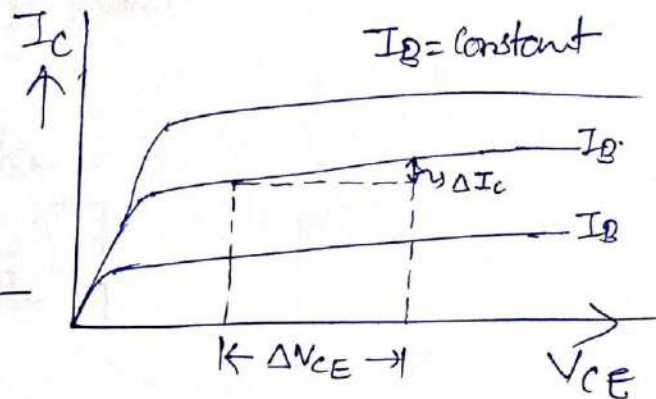

## § Transistor circuit performance in h-parameter

1) Input Impedance: The general expression for input impedance

$$Z_{in} = h_{11} - \frac{h_{12} h_{21}}{h_{22} + \frac{1}{R_L}}$$

by using nomenclature of h parameter for transistor

$$\left[ Z_{in} = h_{ie} - \frac{h_{re} h_{fe}}{h_{oe} + \frac{1}{R_L}} \right]$$

\* Proof: H.W.

2) Current gain: General expression for current gain

$$A_i = \frac{h_{21}}{1 + h_{22} R_L}$$

$$\Rightarrow \left[ A_i = \frac{h_{fe}}{1 + h_{oe} R_L} \right]$$

Proof: H.W.

3) Voltage gain  $A_v$ : General expression

$$A_v = \frac{-h_{21}}{Z_{in} \left( h_{oe} + \frac{1}{R_L} \right)}$$

$$\Rightarrow A_v = \frac{-h_{fe}}{Z_{in} \left( h_{oe} + \frac{1}{R_L} \right)} \quad \text{* Proof = H.W.}$$

4) Output Impedance:  $Z_{out} \rightarrow$  General expression

$$Z_{out} = \frac{1}{h_{22} - \frac{h_{21} h_{12}}{h_{11}}}$$

$$\left[ Z_{out} = \frac{1}{h_{oe} - \frac{h_{fe} h_{re}}{h_{ie}}} \right]$$

Proof: H.W.