

- ① Define Break frequency and unity gain bandwidth.
- ② How can the noninverting amplifier be used as a voltage follower?
- ③ What is the difference between saw tooth and the triangular wave?
- ④ What is an all pass filter? Where and why is it needed?
- ⑤ How can an inverting amp. be used as sign changer? Draw its ckt. diagram.
- ⑥ What is a level translator circuit? Why is it used with cascaded differential amplifier?