

CHAPTER 2


2.1

			<u>TTL JC</u>
(a)	Inverters – 2 pins each	$12/2 = 6$ gates	7404
(b)	2-input XOR – 3 pins each	$12/3 = 4$ gates	7486
(c)	3-input OR – 4 pins each	$12/4 = 3$ gates	
(d)	4-input AND – 5 pins each	$12/5 = 2$ gates	7421
(e)	5-input NOR – 6 pins each	$12/6 = 2$ gates	74260
(f)	8-input NAND – 9 pins	1 gate	7430
(g)	JK flip-flop – 6 pins each	$12/6 = 2$ FFs	74107


2.2

- (a) 74155 – Similar to two decoders as in Fig. 2.2.
- (b) 74157 – Similar to multiplexers of Fig. 2.5.
- (c) 74194 – Similar to register of Fig. 2.9.
- (d) 74163 – Similar to counter of Fig. 2.11

2.3

 


2.4

 

2.5


Remove the inverter from the E input in Fig. 2.2(a).

2.6

 


If all inputs equal 0 or if only $D_0 = 1$:
the outputs $A_2A_1A_0 = 000$.
Needs one more output to recognize
the all zeros input condition.

2.7

 


2.8

 

S_1S_0	$Y_A Y_B$
0 0	$A_0 B_0$
0 1	$A_1 B_1$
1 0	$A_2 B_2$
1 1	$A_3 B_3$

Function table

2.9

 


When the parallel load input = 1, the clock pulses go through the AND gate and the data inputs are loaded into the register when the parallel load input = 0, the output of the AND gate remains at 0.

2.10

The buffer gate does not perform logic. It is used for signal amplification of the clock input.

2.11

 


One stage of Register Fig. 2.7

Load	Clear	D	Operation
0	0	Q(t)	no change
0	1	0	Clear to 0
1	x	I ₀	load I ₀

Function table


2.12

 


2.13

Serial transfer: One bit at a time by shifting. Parallel transfer: All bits at the same time. Input serial data by shifting–output data in parallel. Input data with parallel load–output data by shifting.

2.14

 


2.15

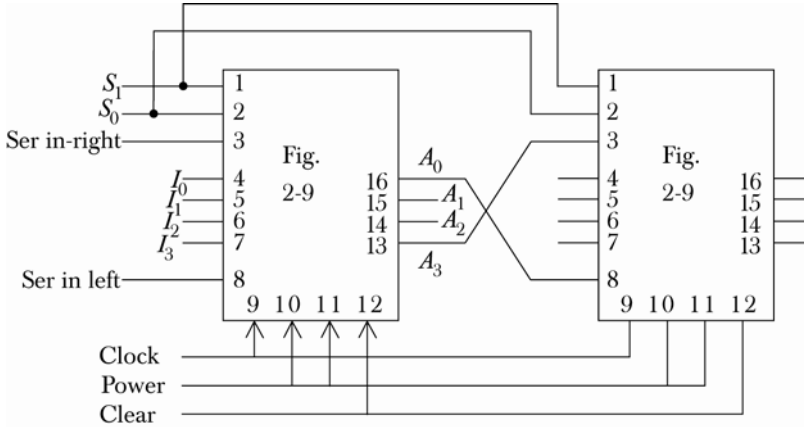


2.16 (a) 4 ; (b) 9

2.17

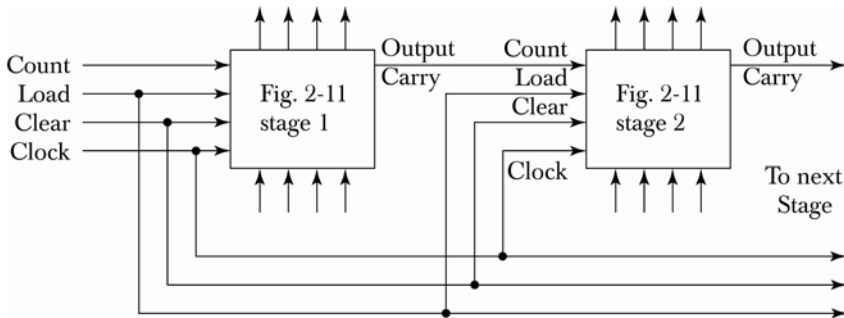

 2.18

After the count reaches $N - 1 = 1001$, the register loads 0000 from inputs.



2.19

- (a) $2K \times 16 = 2^{11} \times 16$
- (b) $64K \times 8 = 2^{16} \times 16$
- (c) $16M \times 32 = 2^{24} \times 32$
- (d) $4G \times 64 = 2^{32} \times 64$


Address lines	Data lines
11	16
16	8
24	32
32	64

2.20

- (a) $2K \times 2 = 4K = 4096$ bytes
- (b) $64K \times 1 = 64K = 2^{16}$ bytes
- (c) $2^{24} \times 4 = 2^{26}$ bytes
- (d) $2^{32} \times 8 = 2^{35}$ bytes

2.21

$$\frac{4096 \times 16}{128 \times 8} = \frac{2^{12} \times 2^4}{2^7 \times 2^3} = 2^6 = 64 \text{ chips}$$

 2.22**2.23**

12 data inputs + 2 enable inputs + 8 data outputs + 2 for power = 24 pins.

CHAPTER 3

3.1

$$(101110)_2 = 32 + 8 + 4 + 2 = 46$$

$$(1110101)_2 = 64 + 32 + 16 + 4 + 1 = 117$$

$$(110110100)_2 = 256 + 128 + 32 + 16 + 4 = 436$$

3.2

$$(12121)_3 = 3^4 + 2 \times 3^3 + 3^2 + 2 \times 3 + 1 = 81 + 54 + 9 + 6 + 1 = 151$$

$$(4310)_5 = 4 \times 5^3 + 3 \times 5^2 + 5 = 500 + 75 + 5 = 580$$

$$(50)_7 = 5 \times 7 = 35$$

$$(198)_{12} = 12^2 + 9 \times 12 + 8 = 144 + 108 + 8 = 260$$

3.3

$$(1231)_{10} = 1024 + 128 + 64 + 15 = 2^{10} + 2^7 + 2^6 + 2^3 + 2^2 + 2 + 1 = (10011001111)_2$$

$$(673)_{10} = 512 + 128 + 32 + 1 = 2^9 + 2^7 + 2^5 + 1 = (1010100001)_2$$

$$(1998)_{10} = 1024 + 512 + 256 + 128 + 64 + 8 + 4 + 2 \\ = 2^{10} + 2^9 + 2^8 + 2^7 + 2^6 + 2^3 + 2^2 + 2^1 = (11111001110)_2$$

3.4

$$(7562)_{10} = (16612)_8$$

$$(1938)_{10} = (792)_{16}$$

$$(175)_{10} = (10101111)_2$$

3.5

$$(F3A7C2)_{16} = (1111\ 0011\ 1010\ 0111\ 1100\ 0010)_2 \\ = (74723702)_8$$

3.6

$$(x^2 - 10x + 31)_r = [(x - 5)(x - 8)]_{10}$$

$$= x^2 - (5 + 8)_{10}x + (40)_{10}$$

$$\text{Therefore: } (10)_r = (13)_{10} \qquad r = 13$$

$$\text{Also } (31)_r = 3 \times 13 + 1 = (40)_{10}$$

$$(r = 13)$$

3.7

$$(215)_{10} = 128 + 64 + 16 + 7 = (11010111)_2$$

$$(a) \quad 000011010111 \qquad \text{Binary}$$

$$(b) \quad \begin{array}{cccc} 000 & 011 & 010 & 111 \\ 0 & 3 & 2 & 7 \end{array} \quad \text{Binary coded octal}$$

$$(c) \quad \begin{array}{ccc} 0000 & 1101 & 0111 \\ 0 & D & 7 \end{array} \quad \text{Binary coded hexadecimal}$$

$$(d) \quad \begin{array}{ccc} 0010 & 0001 & 0101 \\ 2 & 1 & 5 \end{array} \quad \text{Binary coded decimal}$$

3.8

$$(295)_{10} = 256 + 32 + 7 = (100100111)_2$$

$$(a) \quad 0000\ 0000\ 0000\ 0001\ 0010\ 0111$$

$$(b) \quad 0000\ 0000\ 0000\ 0010\ 1001\ 0101$$

$$(c) \quad 10110010\ 00111001\ 00110101$$

3.10

JOHN DOE

3.11

87650123; 99019899; 09990048; 999999.

3.12

876100; 909343; 900000; 000000

3.13

01010001; 01111110; 01111111; 11111110; 11111111
 01010010; 01111111; 10000000; 11111111; 00000000

3.14

(a)	5250	(b)	1753	(c)	020	(d)	1200
	+ 8679		+ 1360		+ 900		+ 9750
	<u>1)3929</u>		<u>0)3113</u>		<u>0)920</u>		<u>1)0950</u>
			↓ = 10's complement □				
			- 6887		- 080		

3.15

(a)	(b)	(c)	(d)
11010	11010	000100	1010100
+10000	+10011	+ 010000	+ 0101100
<u>1)01010</u>	<u>1)01101</u>	<u>0)010100</u>	<u>1)0000000</u>
		↓	
(26 - 16 = 10)	(26 - 13 = 13)	-101100	(84 - 84 = 0)
		(4 - 48 = -44)	

3.16

+ 42 = 0101010	+13 = 0001101
- 42 = 1010110	-13 = 1110011
(+42) 0101010	(- 42) 1010110
<u>(-13) 1110011</u>	<u>(+ 13) 0001101</u>
(+29) 0011101	(- 29) 1100011


3.17 01 ← last two carries → 1 0

+ 70	01000110	- 70	10111010
+ 80	<u>01010000</u>	- 80	<u>10110000</u>
+150	10010110	- 150	01101010
↑	↑	↑	↑
greater	negative	less than	positive
than		- 128	
+127			

3.18

(a)	(-638)	9362	(b)	(-638)	9362
	<u>(+785)</u>	+ <u>0785</u>		<u>(-185)</u>	+ <u>9815</u>
	(+147)	0147		(-823)	9177

3.19

 

3.20

$$46.5 = 32 + 8 + 4 + 2 + 0.5 = (101110.1)_2$$

Sign

0101110100000000

24-bit mantissa

00000110

8-bit exponent (+6)

3.21 (a)

Decimal	Gray code
16	11000
17	11001
18	11011
19	11010
20	11110
21	11111
22	11101
23	11100
24	10100
25	10101
26	10111
27	10110
28	10010
29	10011
30	10001
31	10000

(b)

Decimal	Excess-3	Gray
9	0010	1010
10	0110	1010
11	0110	1110
12	0110	1111
13	0110	1101
14	0110	1100
15	0110	0100
16	0110	0101
17	0110	0111
18	0110	0110
19	0110	0010
20	0111	0010

3.22 8620

- (a) BCD 1000 0110 0010 0000
- (b) XS-3 1011 1001 0101 0011
- (c) 2421 1110 1100 0010 0000
- (d) Binary 10000110101100 (8192 + 256 + 128 + 32 + 8 + 4)

3.23

<u>Decimal</u>	<u>BCD with even parity</u>	<u>BCD with odd parity</u>
0	00000	10000
1	10001	00001
2	10010	00010
3	00011	10011
4	10100	00100
5	00101	10101
6	00110	10110
7	10111	00111
8	11000	01000
9	01001	11001

3.24

$$3984 = 0011 \ 1111 \ 1110 \ 0100$$

$$= 1100 \ 0000 \ 0001 \ 1011 = 6015$$

3.25

<u>A B</u>	<u>Y = A ⊕ B</u>
0 0	0
0 1	1
1 0	1
1 1	0

<u>C D</u>	<u>Z = C ⊕ D</u>
0 0	0
0 1	1
1 0	1
1 1	0

<u>y</u>	<u>z</u>	<u>x = y ⊕ z</u>
0	0	0
0	1	1 ←
1	0	1 ←
1	1	0

ABCD

0001, 0010, 1101, 1110

0100, 0111, 1000, 1011

Always odd number of 1's

3.26

Same as in Fig. 3.3 but without the complemented circles in the outputs of the gates.

$$P = x \oplus y \oplus z$$

$$\text{Error} = x \oplus y \oplus z \oplus P$$