



Learning Outcomes

Understand Linear Network

Differentiate between unilateral and bilateral Network

Understand the importance of Thevenin's
theorem

Draw Complex Network into a Thevenin's equivalent circuit

Thevenin's Theorem

Any Linear and bilateral Electric Network or complex circuit with Current and Voltage sources can be replaced by an equivalent circuit containing of a single independent open circuit thevenin's voltage Source V_{TH} in Series with the thevenin's Resistance R_{TH} .along with the load resistance R_L



STEP 6

STEP 5

STEP 4

STEP 3

STEP 2

STEP 1

Thevenin's Theorem

STEP 6

STEP 5


STEP 4

STEP 3


STEP 2

STEP 1

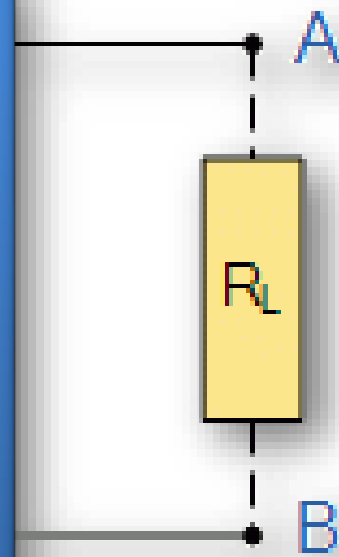Any linear and bilateral network containing several current and voltage sources & resistances



=

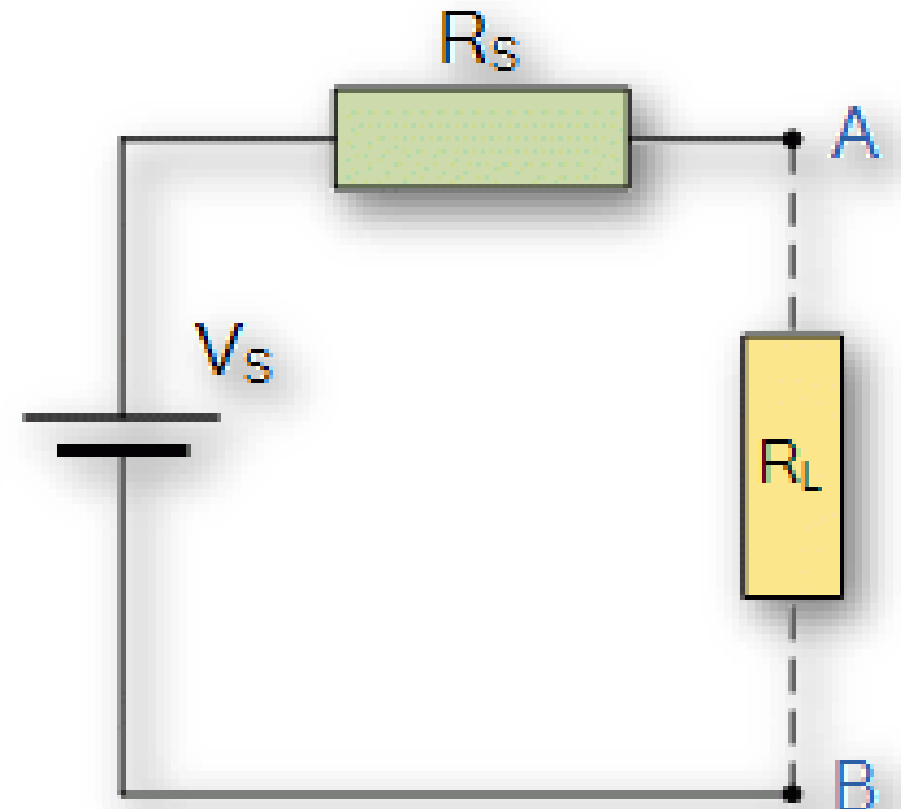

Find the load resistor



STEP 6

STEP 5



STEP 4

STEP 3

STEP 2

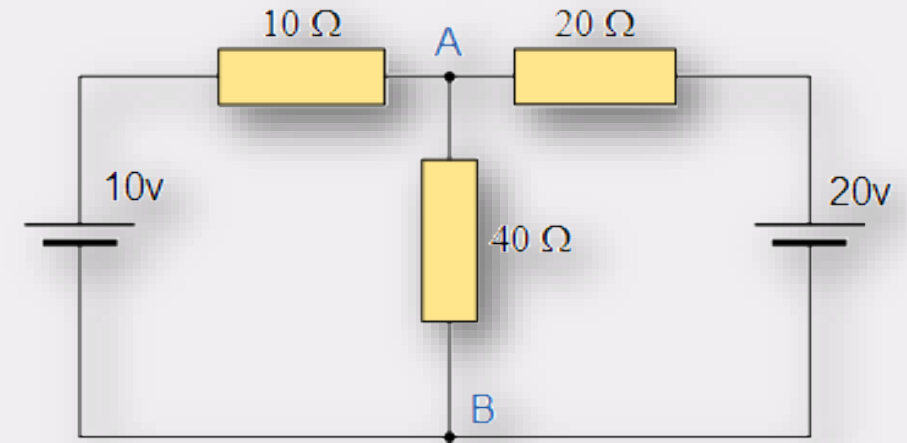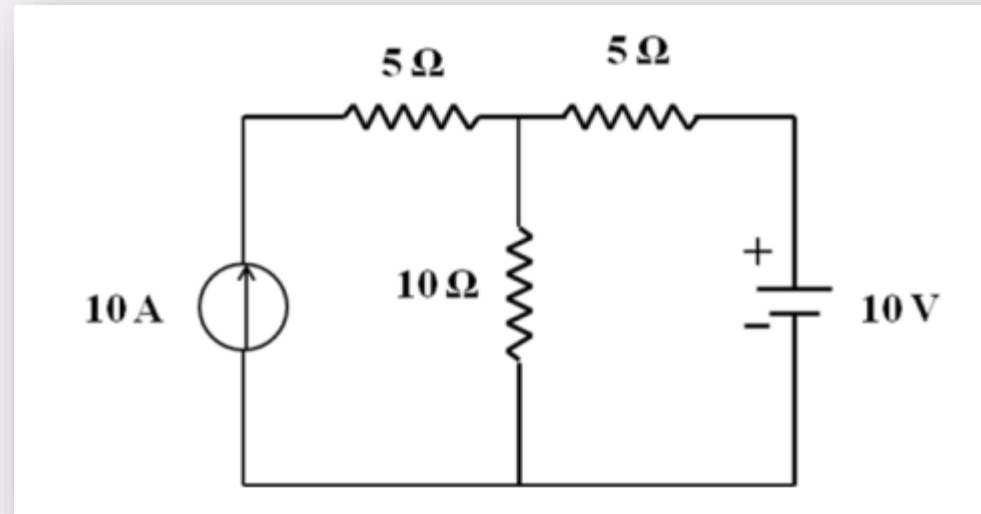

STEP 1

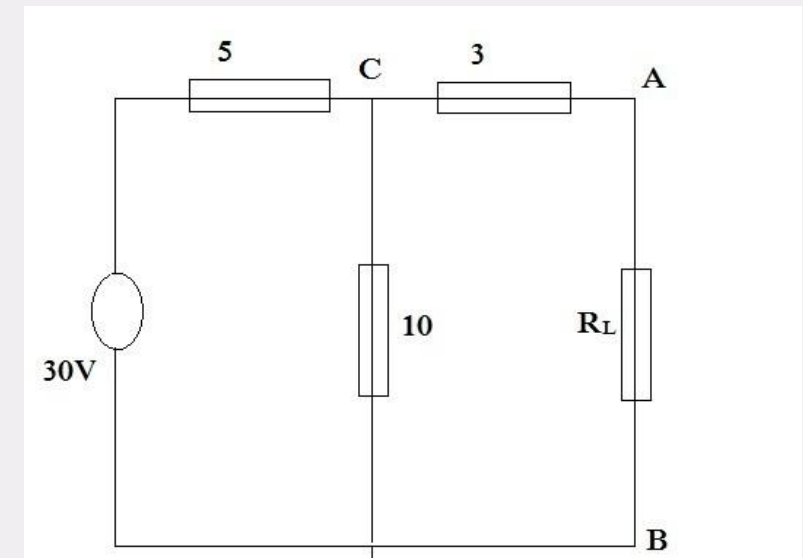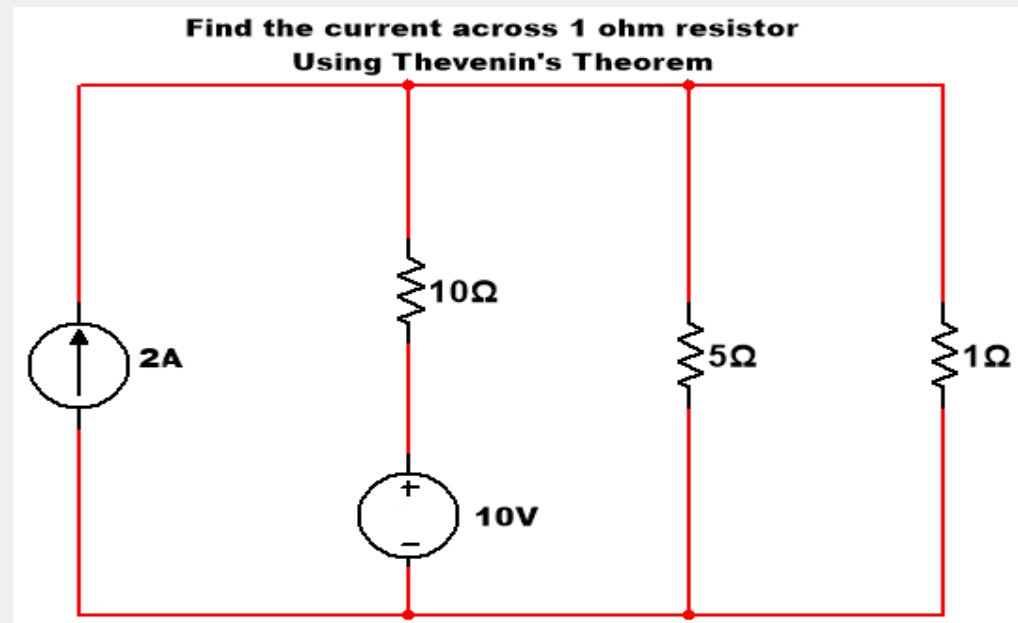

STEP 6

STEP 5

STEP 4

STEP 3

Remove the Load Resistance R_L
Calculate/measure the open circuit Thevenin's voltage V_{TH} across two open ends



STEP 2

STEP 1

STEP 6

STEP 5

STEP 4

Remove the Load Resistance R_L
**Replace all active sources with their internal
resistance**



STEP 3

STEP 2

STEP 1

STEP 6

STEP 5

Remove the Load Resistance R_L
Calculate /measure the equivalent Thevenin's
Resistance R_{TH} Across two open ends



STEP 4

STEP 3

STEP 2

STEP 1

STEP 6

Now, Draw the equivalent circuit for given network

This is the Equivalent Thevenin's Circuit



STEP 5

STEP 4

STEP 3

STEP 2


STEP 1

Now find the Load current flowing through the Load Resistor by using given identity


$$I_L = V_{TH} / (R_{TH} + R_L)$$



Example -1

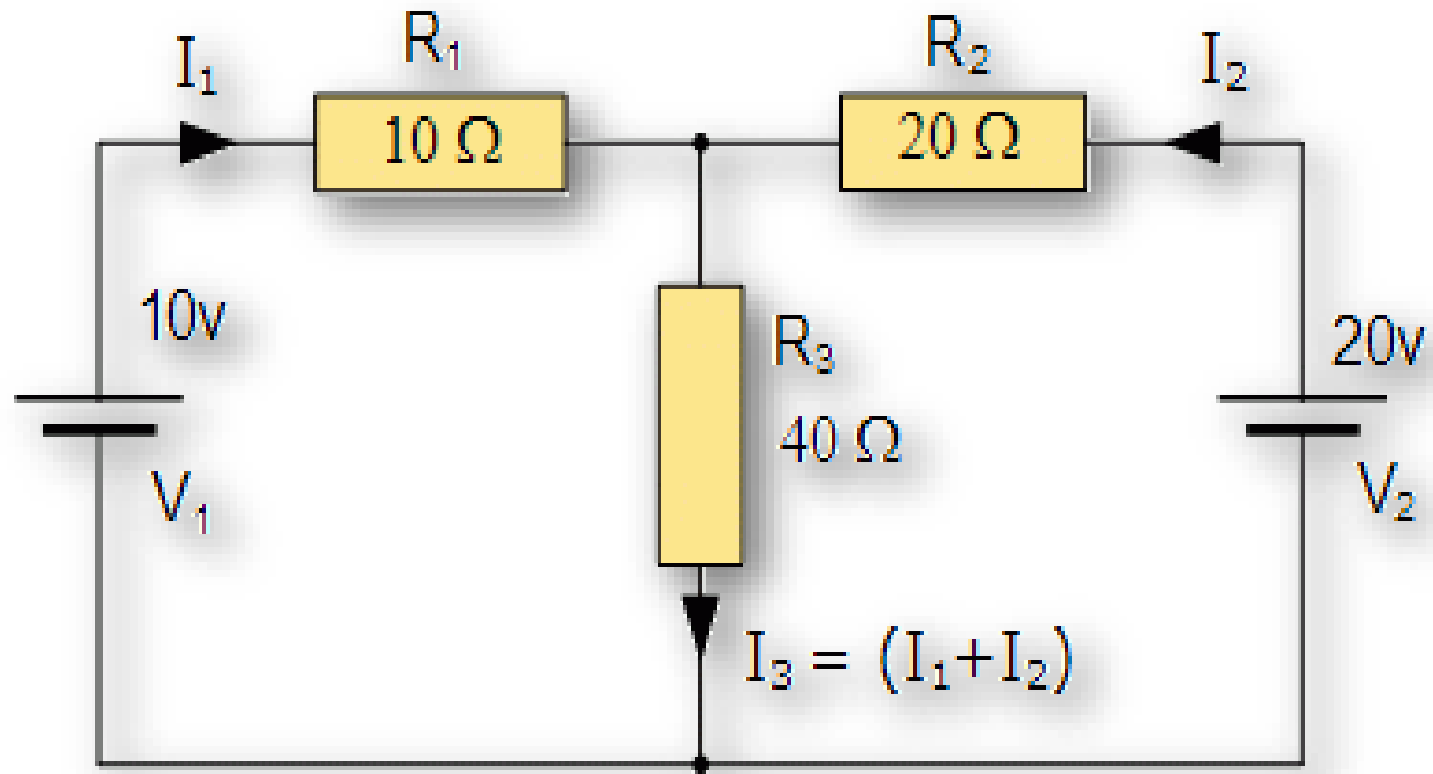


Step -1

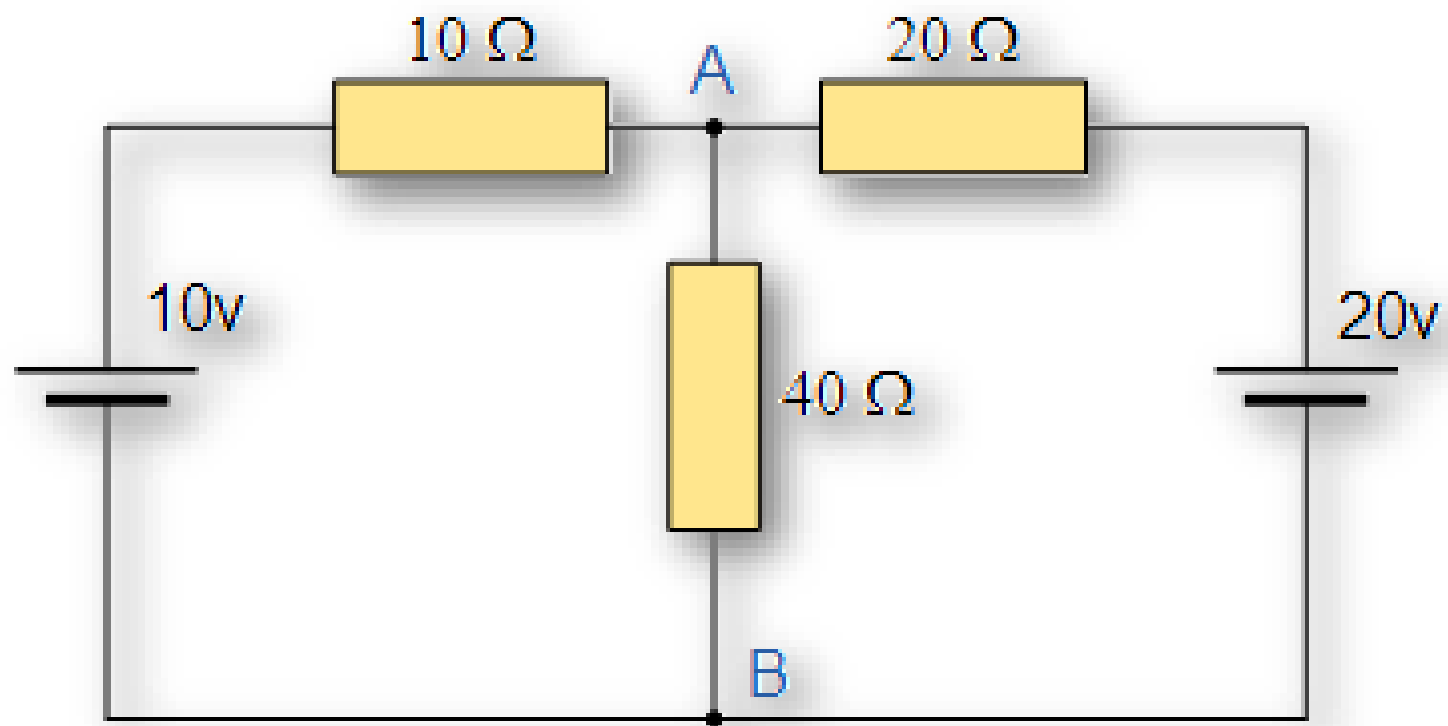

$$R_L = 40 \Omega$$

Step - 2

Calculate V_{TH}

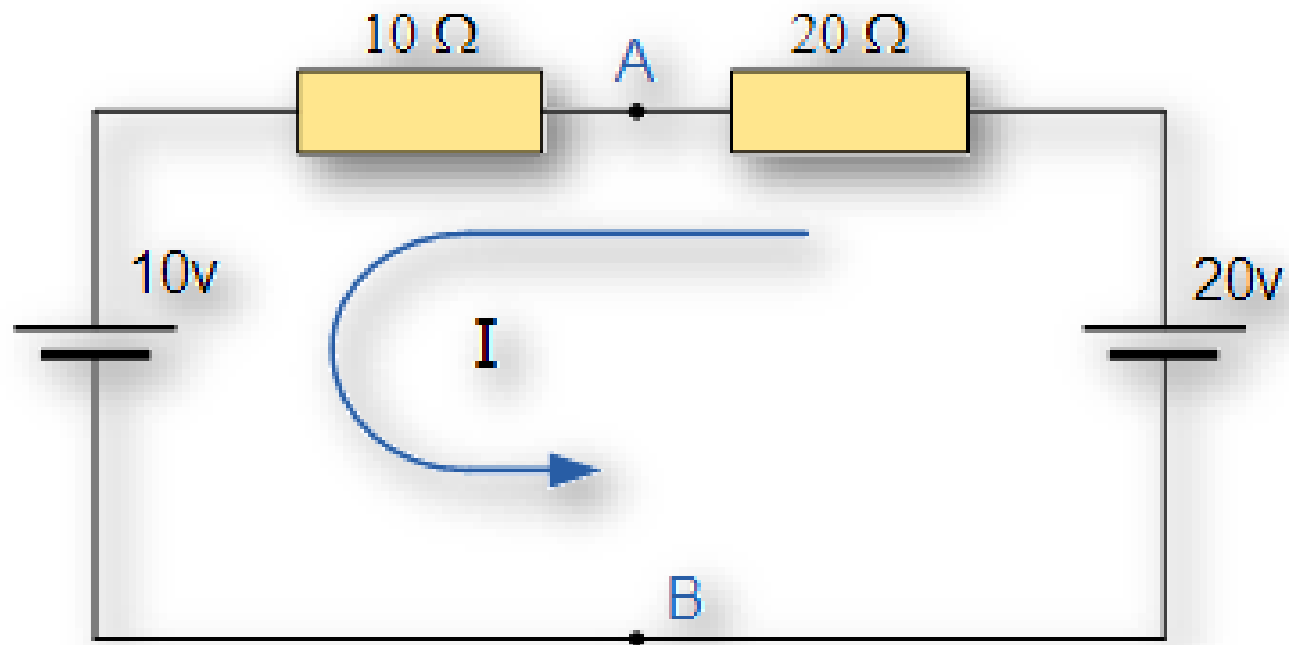


The current flowing around the loop :

$$I = \frac{V}{R} = \frac{20v - 10v}{20\Omega + 10\Omega} = 0.33 \text{ amps}$$

Step -2

Calculate V_{TH}

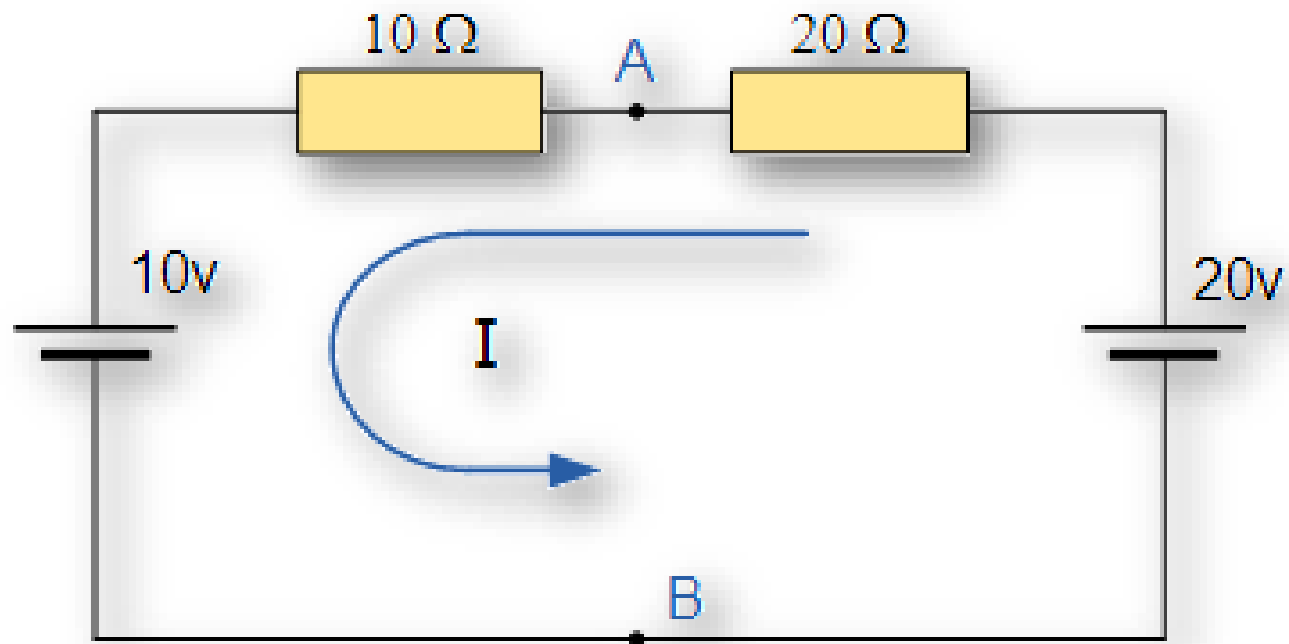

The current flowing around the loop :

$$I = \frac{V}{R} = \frac{20v - 10v}{20\Omega + 10\Omega} = 0.33 \text{ amps}$$


This current of 0.33 amperes is common to both voltage drop across the 20Ω resistor

$$V_{AB} = 20 - (20\Omega \times 0.33\text{amps}) = 13.33 \text{ volts}$$

.

Step -1, 2

Calculate V_{TH}

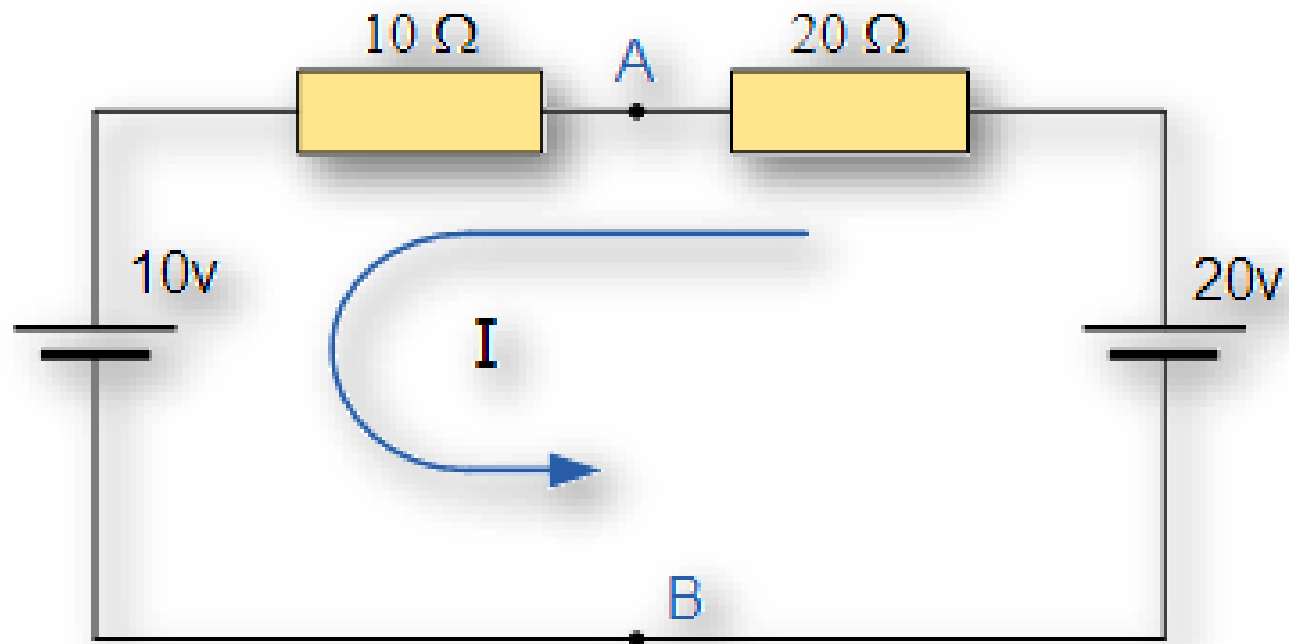

The current flowing around the loop :

$$I = \frac{V}{R} = \frac{20v - 10v}{20\Omega + 10\Omega} = 0.33 \text{ amps}$$


This current of 0.33 amperes is common to both voltage drop across the 20Ω resistor

$$V_{AB} = 20 - (20\Omega \times 0.33\text{amps}) = 13.33 \text{ volts}$$


Or across the 10Ω resistor :

$$V_{AB} = 10 + (10\Omega \times 0.33\text{amps}) = 13.33 \text{ volts,}$$

Step - 3

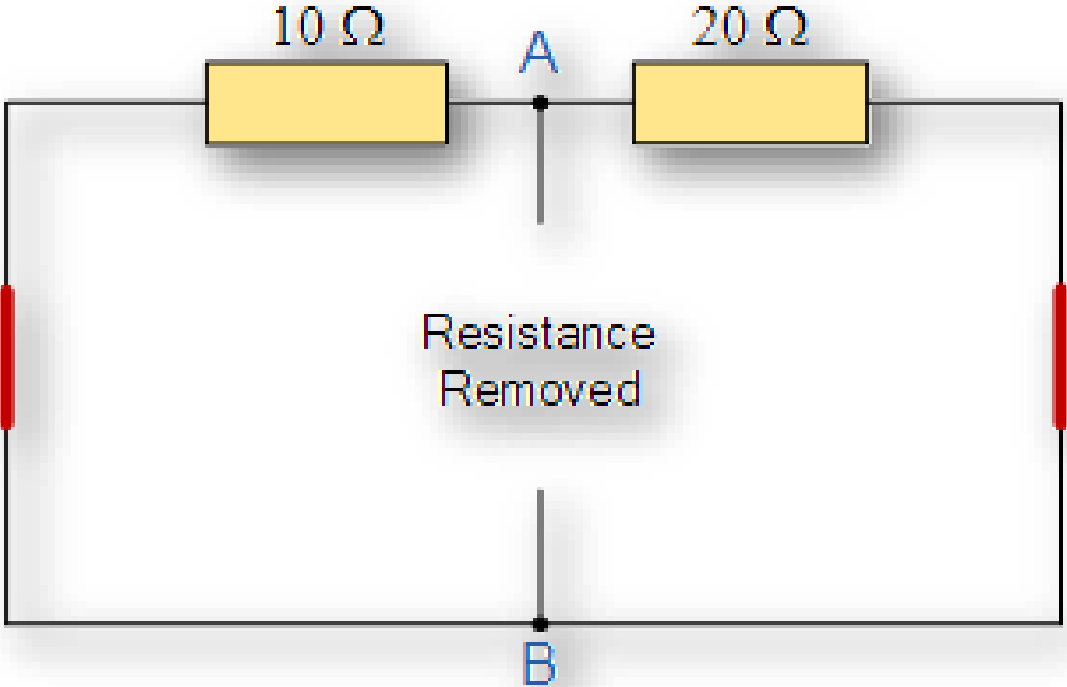



Step - 4 Find R_{TH}

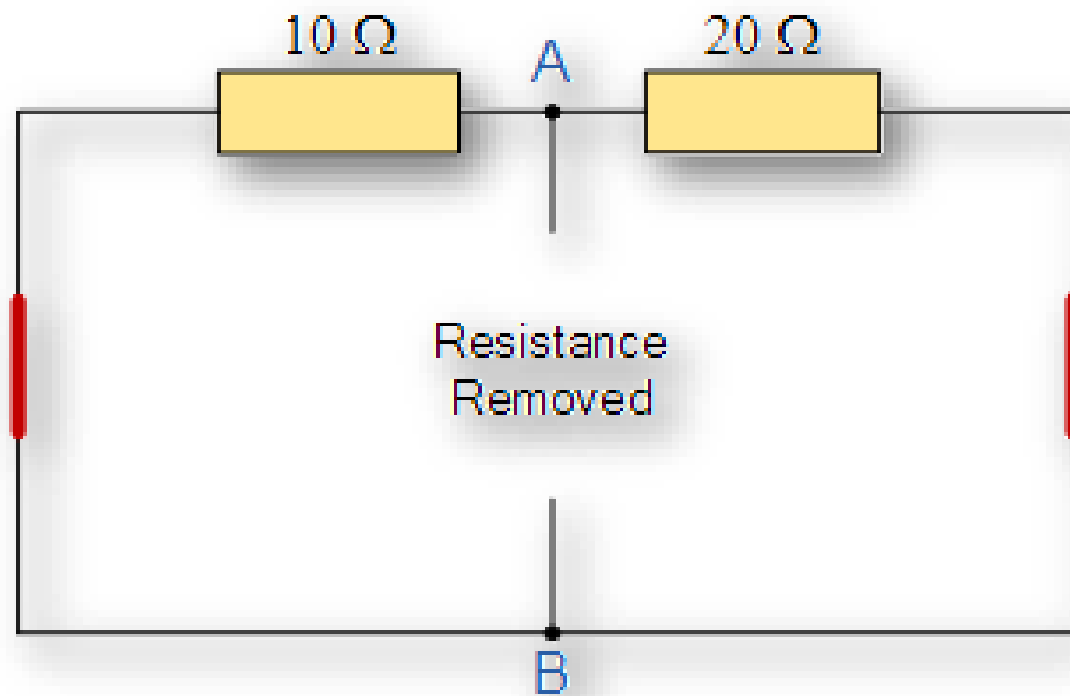


$10\ \Omega$ Resistor in Parallel with the $20\ \Omega$ Resistor

$$R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{20 \times 10}{20 + 10} = 6.67\ \Omega$$

Step - 5

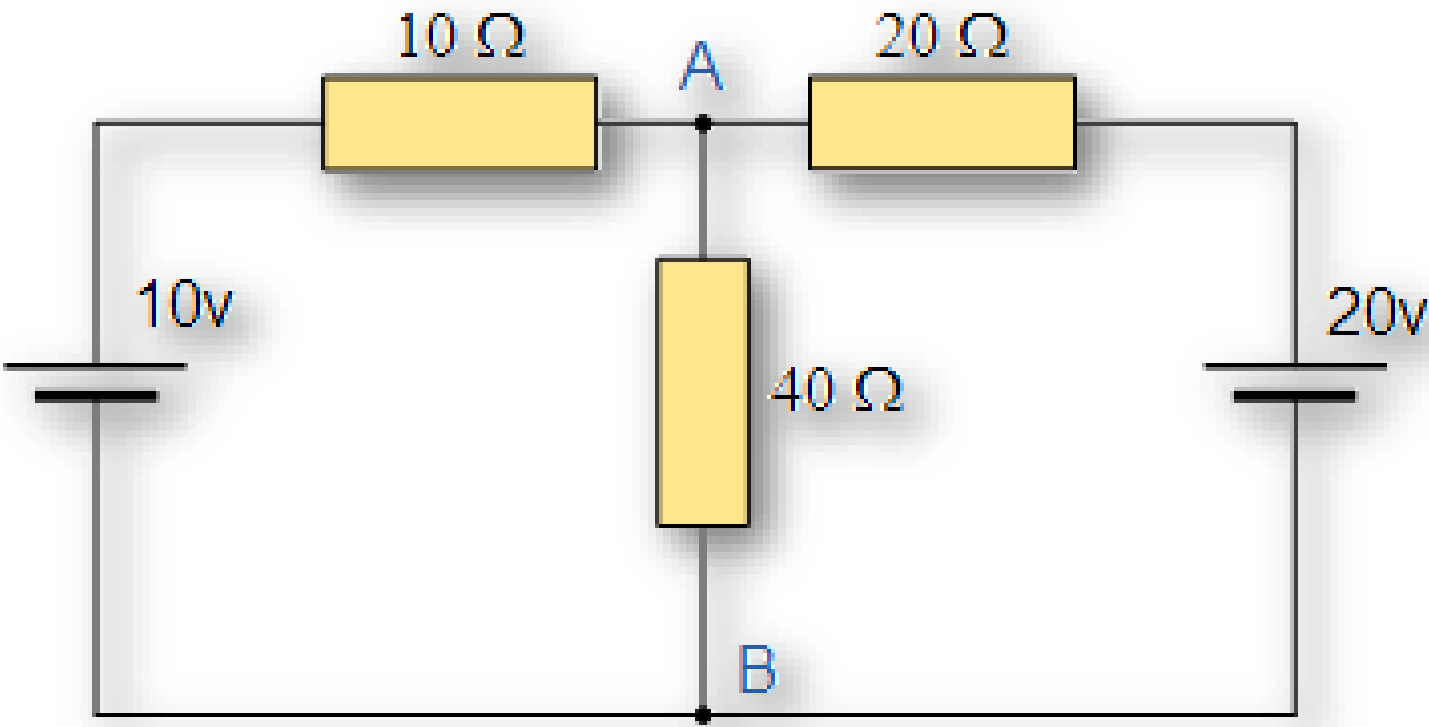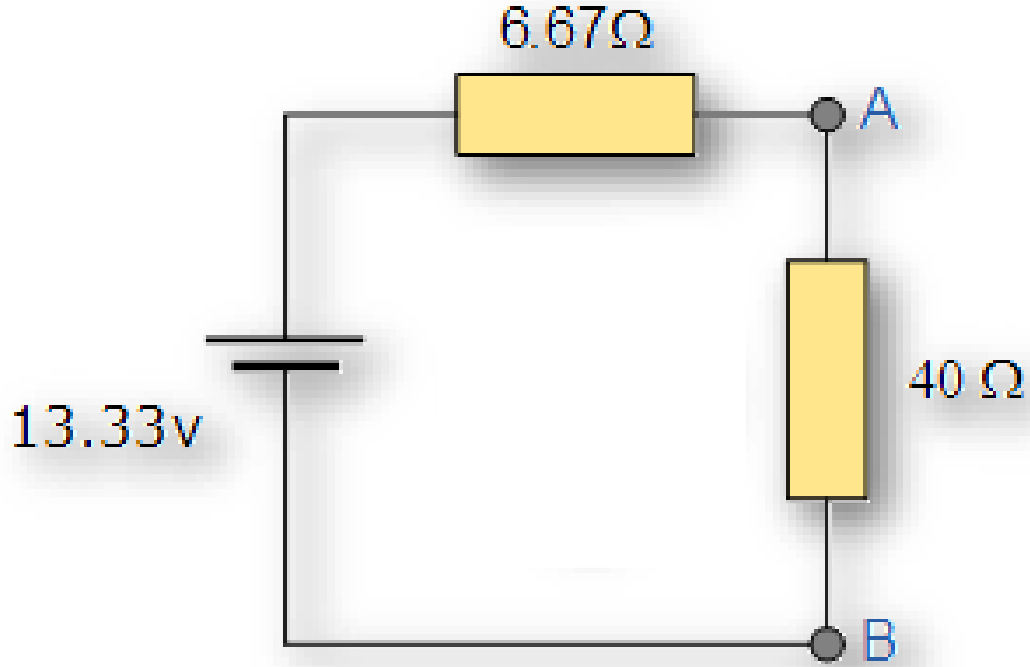


Step - 6

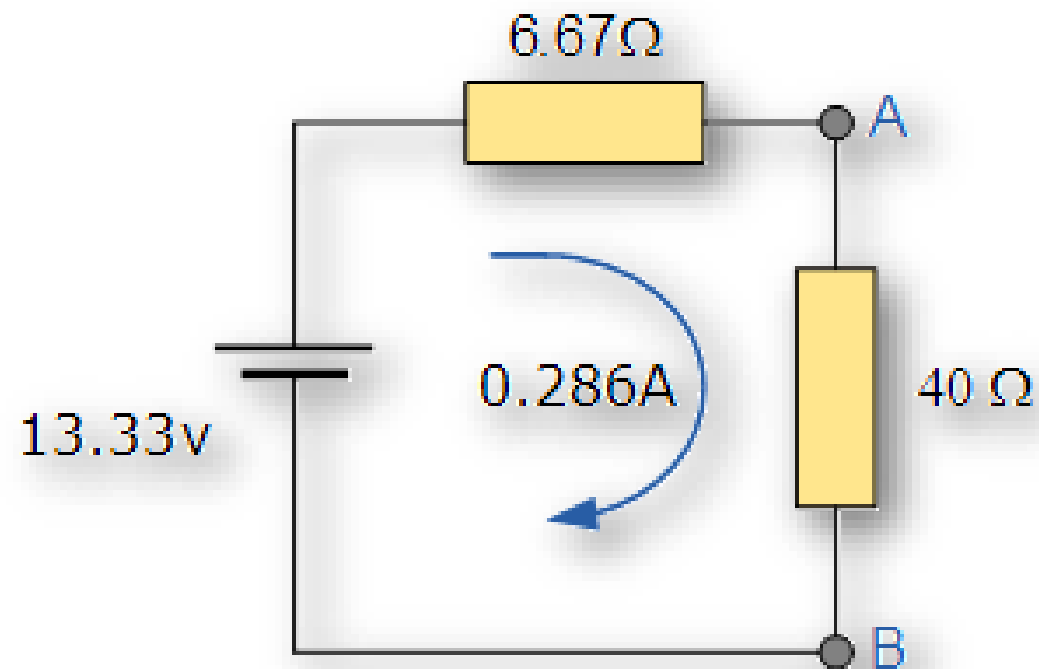

$$I = \frac{V}{R} = \frac{13.33 \text{ v}}{6.67\Omega + 40\Omega} = 0.286 \text{ amps}$$

Same as found using [Kirchhoff's circuit law](#)


Example -2

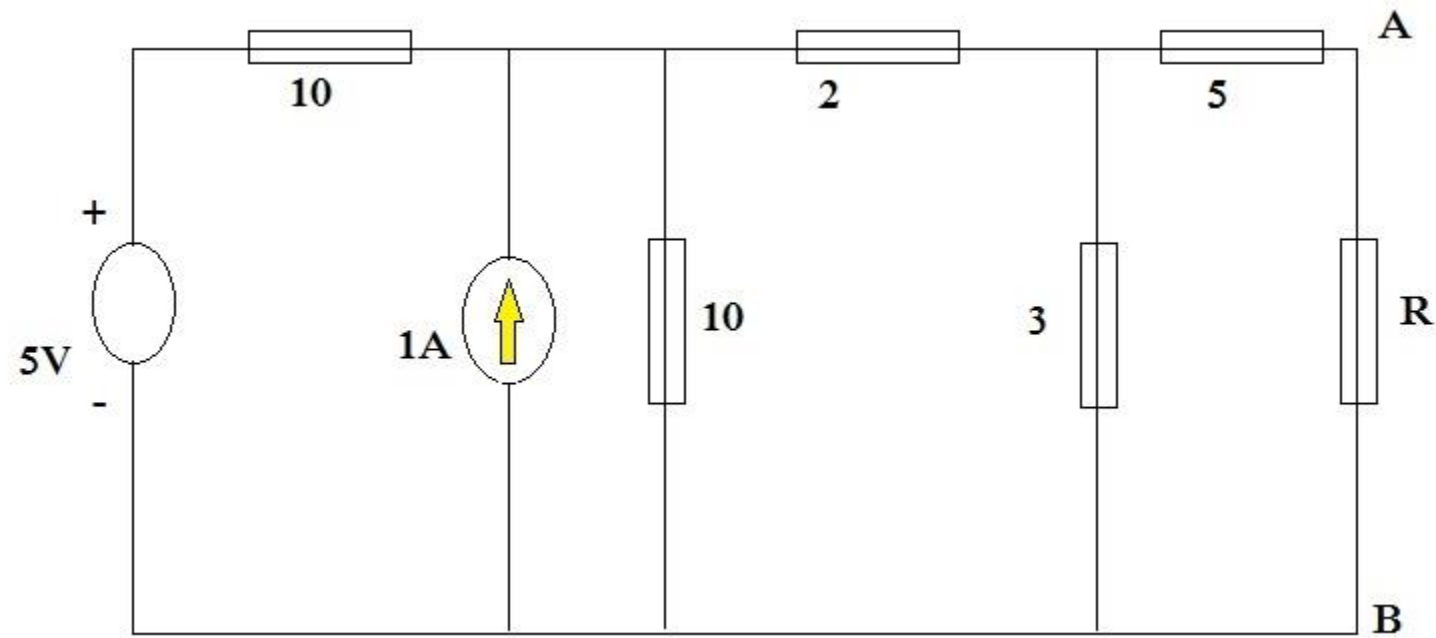

Determine the thevenin's equivalent circuit between the terminals A&B.

Given $R = 5 \Omega$


Step -1 R_L ?

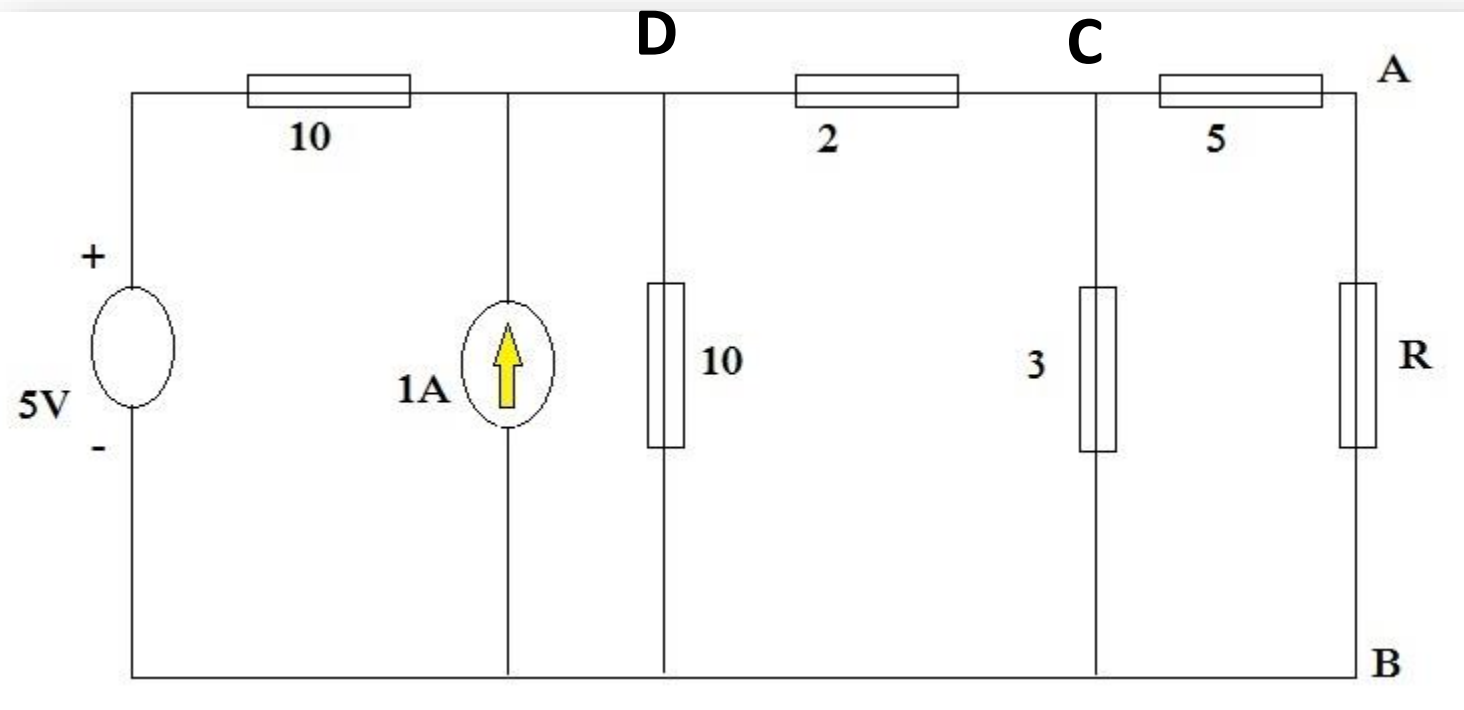

Find the value of R_L


R_L is given $R = 5 \Omega$

Step -2 Remove R_L

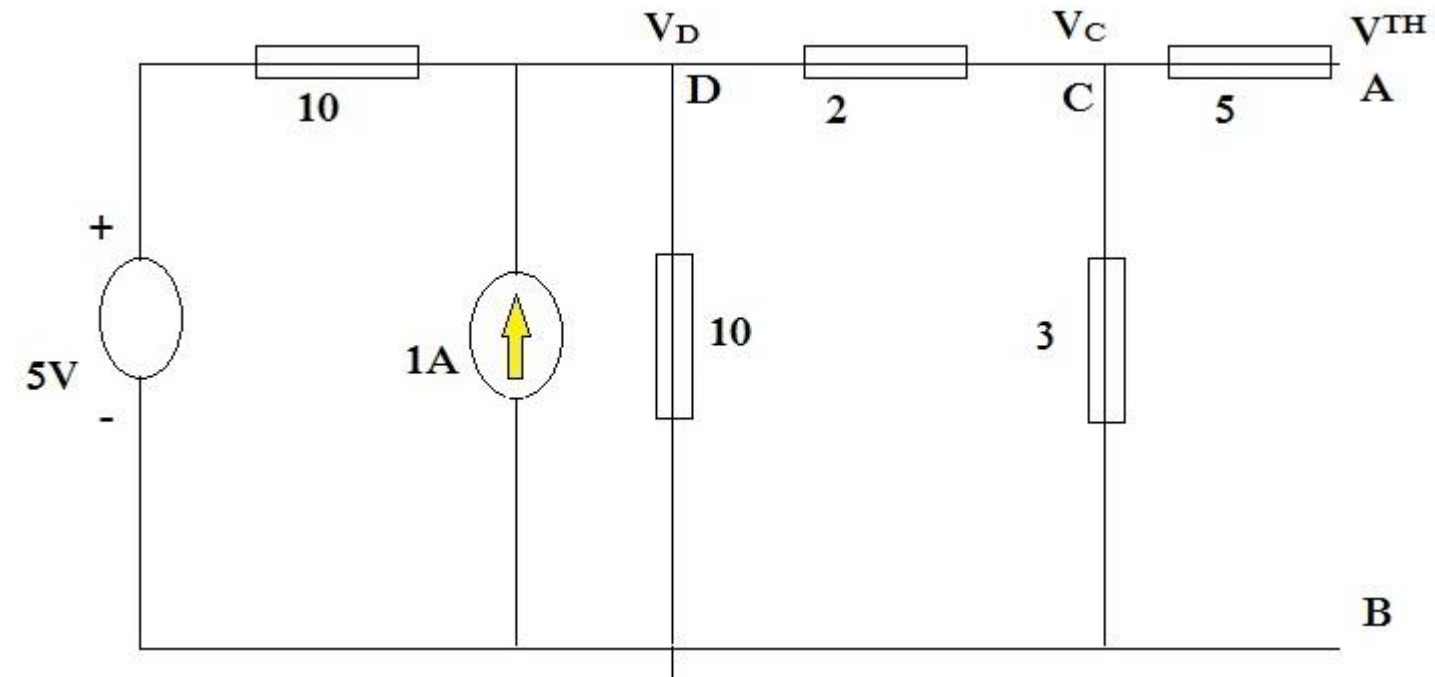

Voltage at point C = $V_C = V^{th}$ (as there is no current through 5Ω resistor)

Step -2 Calculate V_{TH}

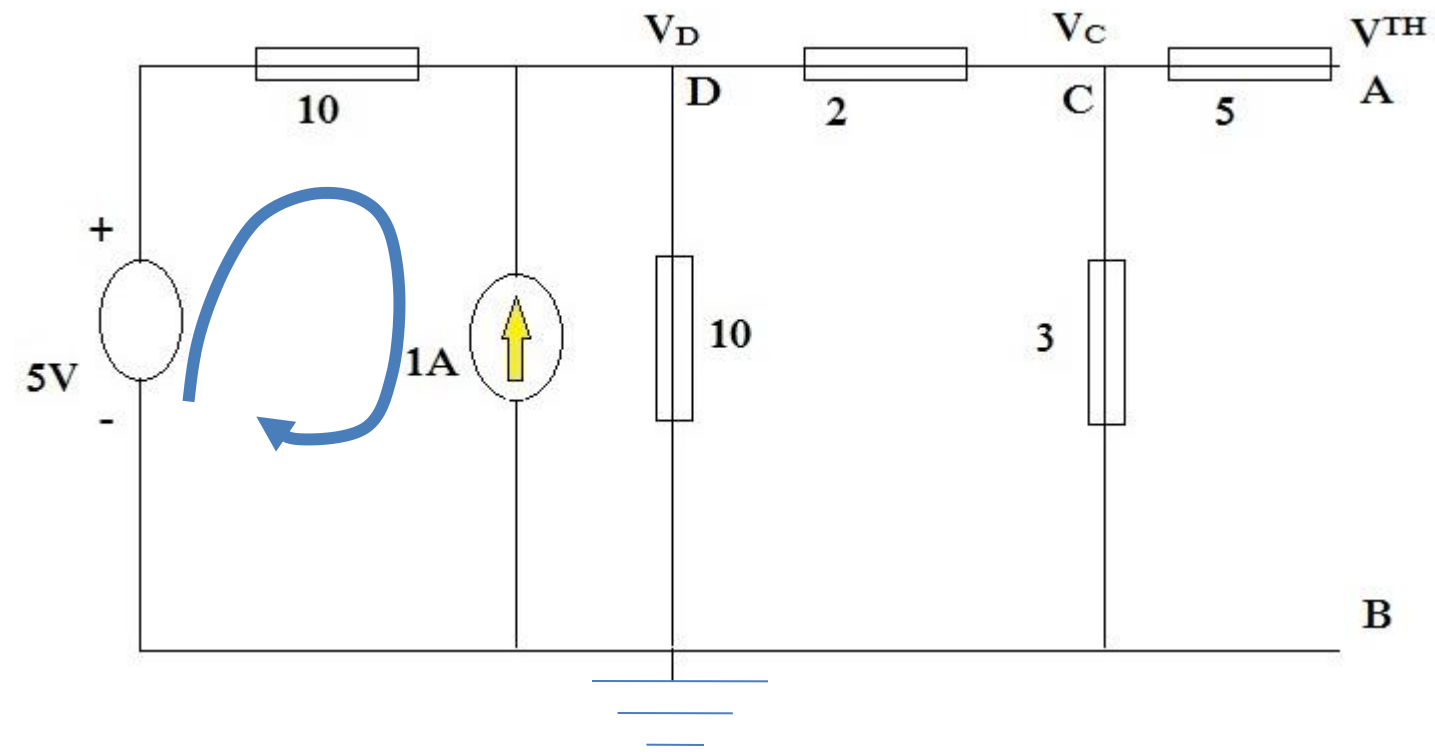

Grounded the point B

Applying KCL at Nodes C and D

Nodal equation to point C

$$(V_C - 0)/3 + (V_C - V_D)/2 = 0$$

$$5V_C - 3V_D = 0 \text{ -----(1)}$$

Nodal equation to point D

$$(V_D - V_C)/2 + (V_D - 0)/10 + (V_D - 5)/10 - 1 = 0$$

$$7V_D - 5V_C = 15 \text{ -----(2)}$$


By solving 1&2

$$V_C = 2.25V$$


$$V_C = V^{TH}$$

$$\mathbf{V^{TH} = 2.25V}$$

Step - 3

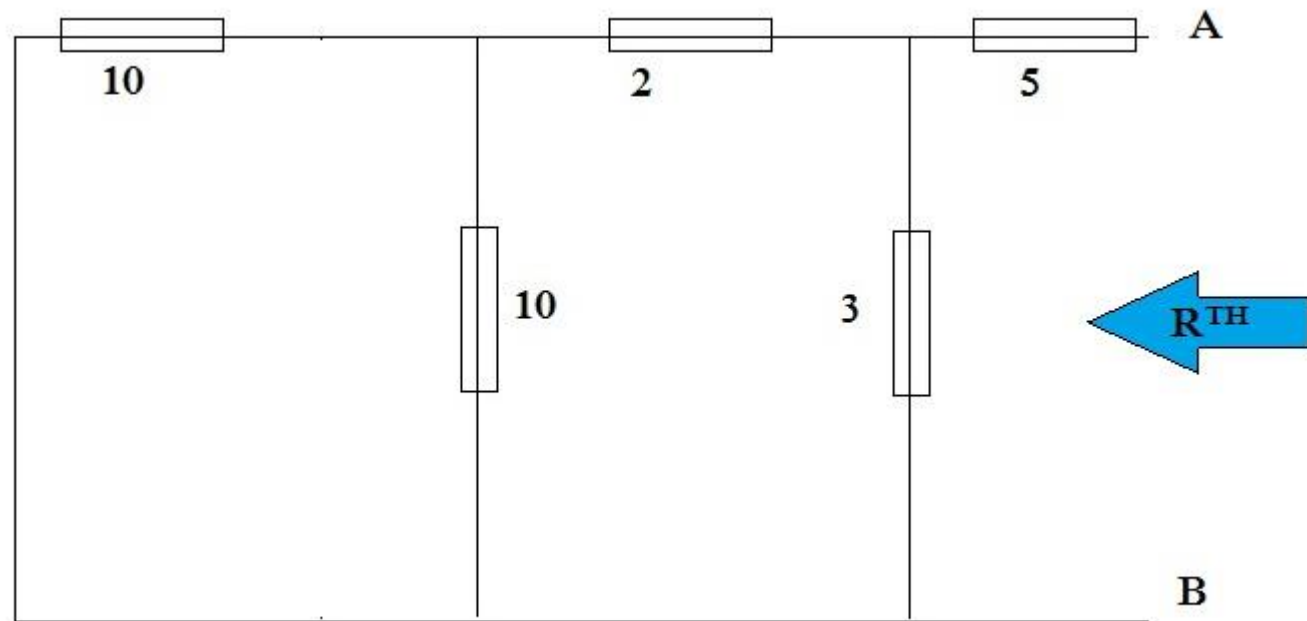


Step - 4 Find R_{TH}

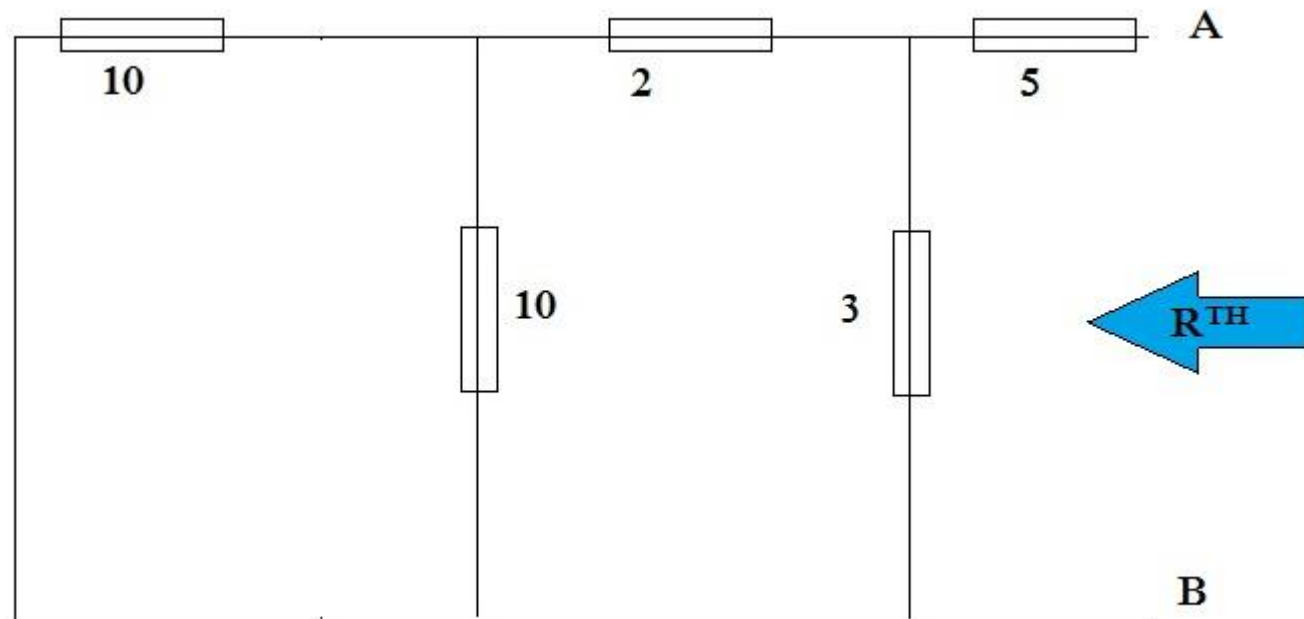


$$R^{TH} = 5 + \{ [(10 // 10) + 2] // 3 \}$$

$$\underline{\underline{R^{TH} = 7.1 \Omega}}$$

Step - 5

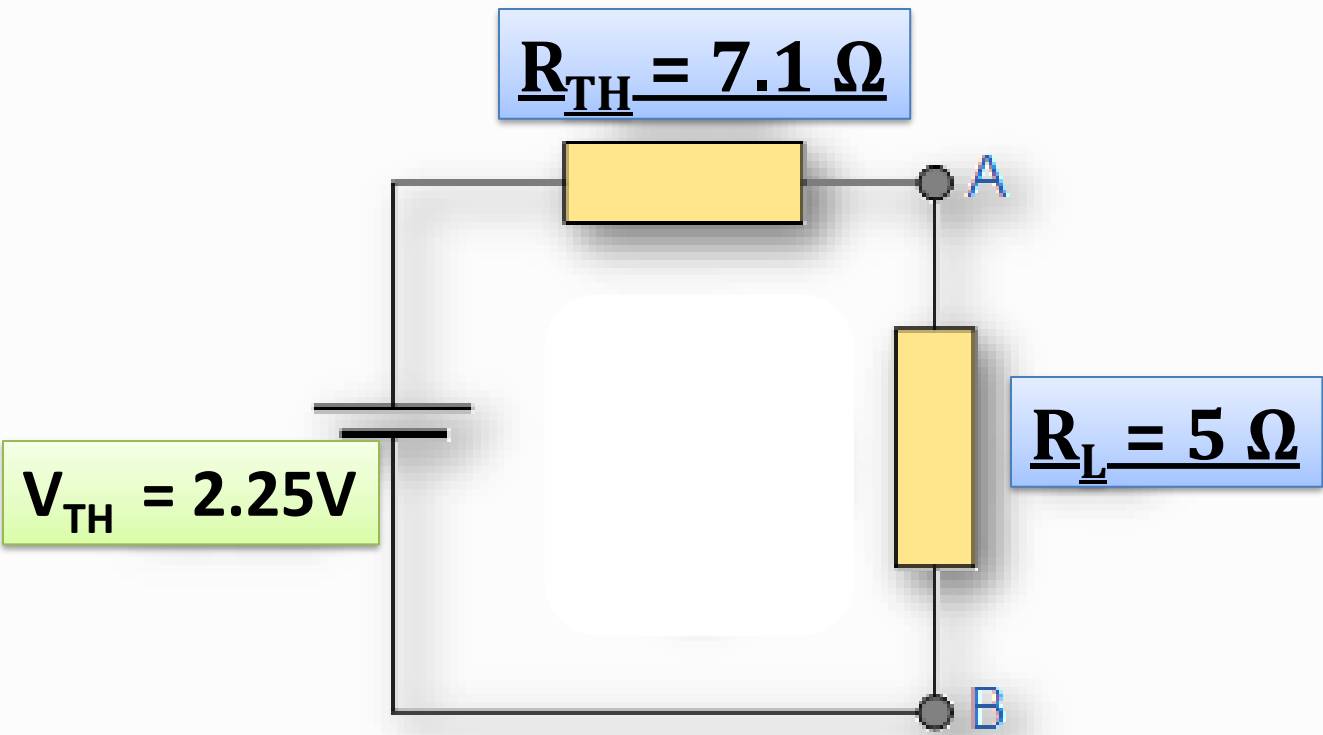

Step - 6

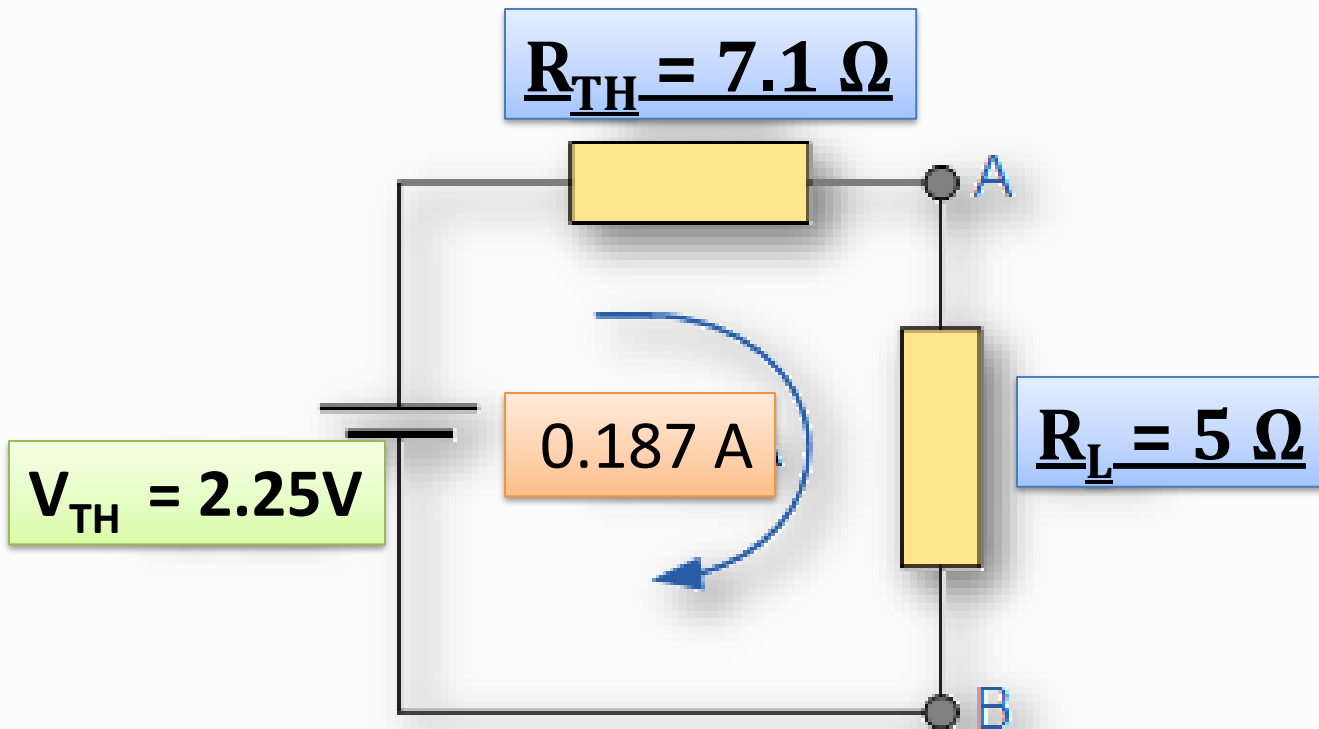


$$I = V / (R_{TH} + R_L)$$

$$I = 2.26 / (7.1 + 5)$$


$$I = 0.187 A$$

Example -3

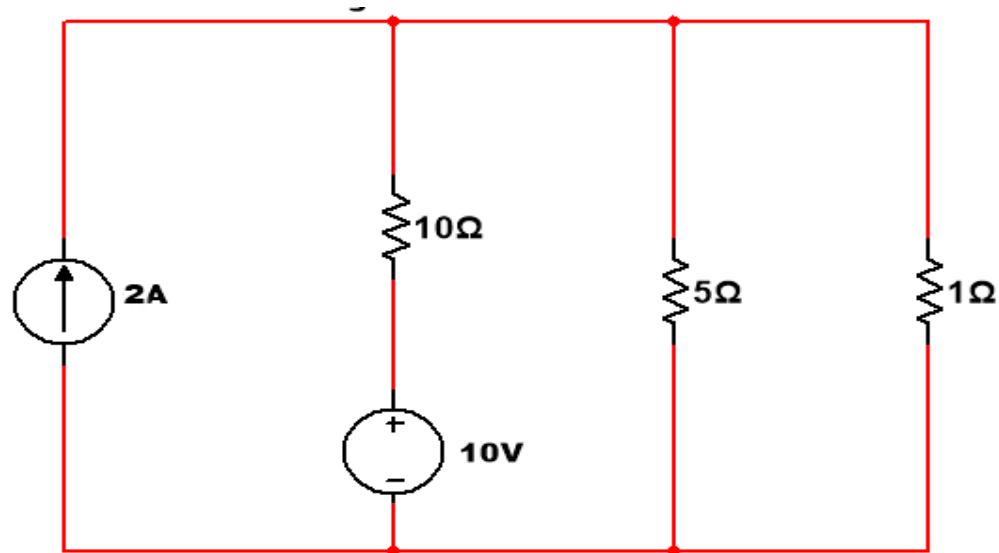

Find the value of current through 1Ω Resistor in the given circuit using Thevenin's theorem.

Step -1 R_L ?

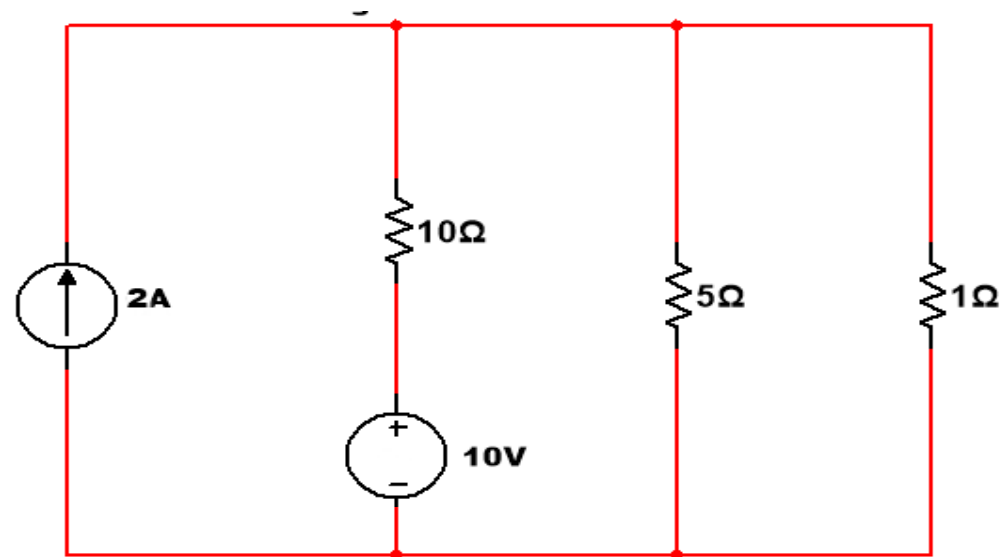

Find the value of R_L

$$R_L = 1 \Omega$$

Step -2 Calculate V_{TH}

Applying KVL in All meshes.

Mesh 1

$$I_1 = 2A$$

$$\text{Mesh 2 } -10 + 10 I_2 - 10 I_1 + 5 I_2 = 0$$

Solve

$$15 I_2 - 10 I_1 = 10$$


$$15 I_2 = 10 + 20$$

$$I_2 = \frac{30}{15} = 2A$$


The voltage across the 5Ω resistor

$$\text{is } V = I * R = 2 * 5 = 10 V$$


$$\text{So } V_{TH} = 10 V$$

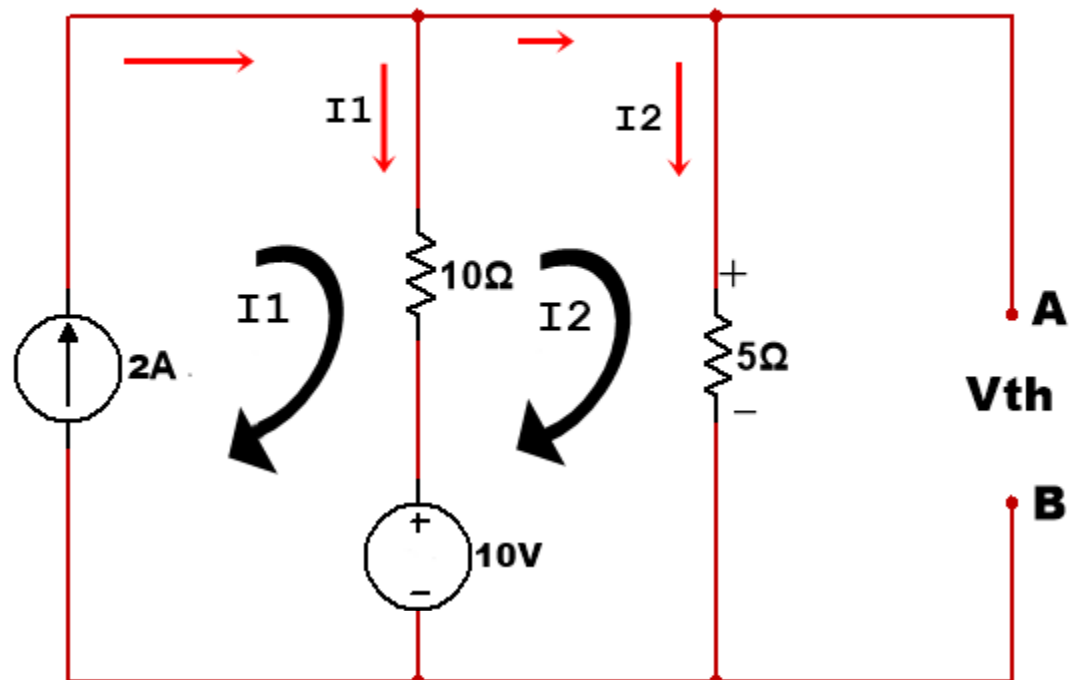

Step - 3

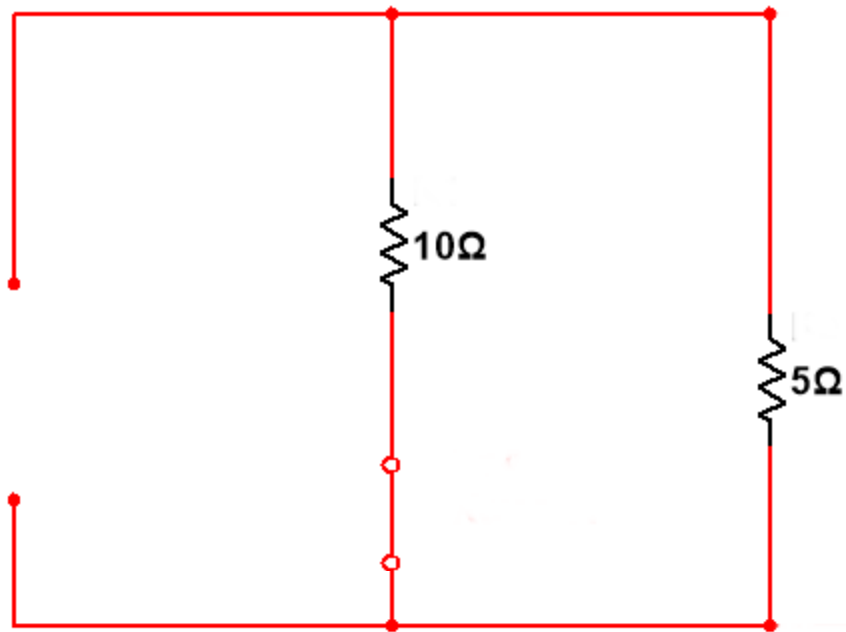


Step - 4 Find R_{TH}

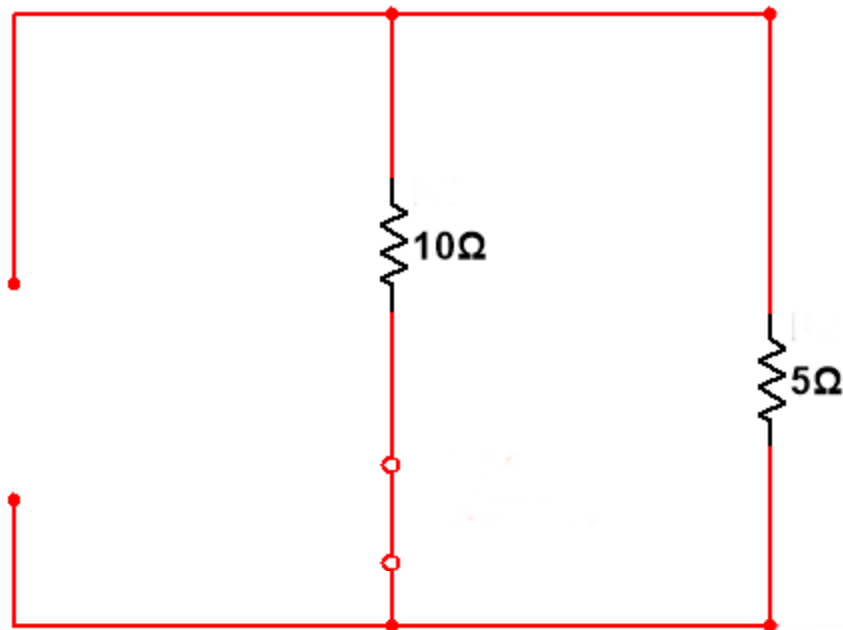


$$R_{TH} = 10\Omega // 5\Omega$$

$$R_{TH} = 3.33\Omega$$

Step - 5

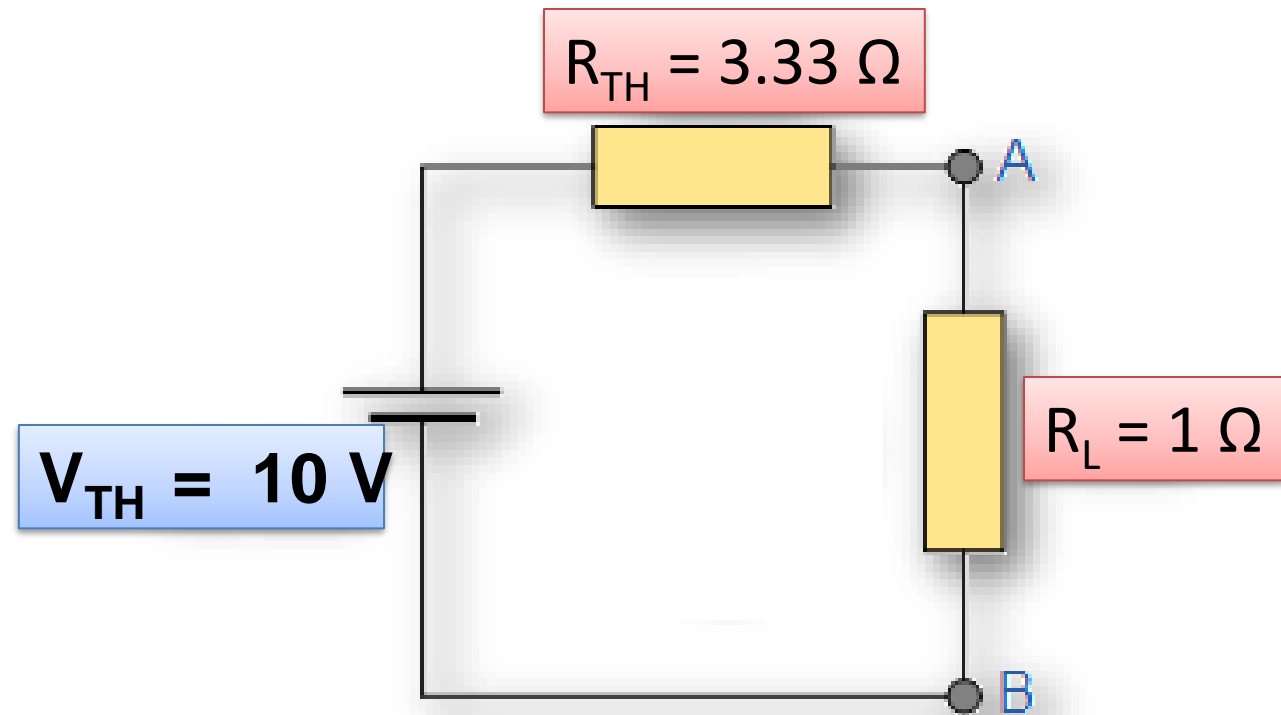

Step - 6

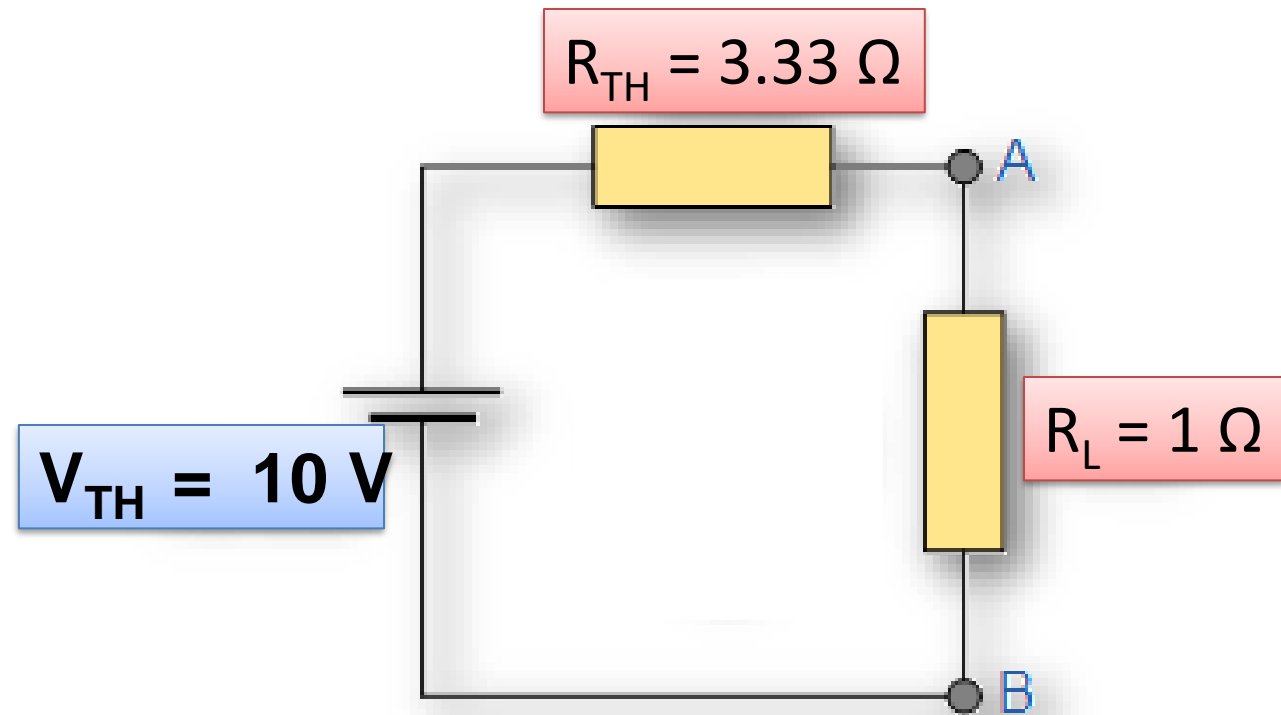

$$I = V / (R_{TH} + R_L)$$

$$I = 10 / (3.33 + 1)$$

$$I = 2.31\ \text{A}$$